

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

$$\frac{Y(s)}{X(s)} = \frac{P_1\Delta_1 + P_2\Delta_2}{\Delta}$$
$$\frac{Y(s)}{X(s)} = \frac{G_1 + G_2}{1 + G_1H}$$

Hence, the correct option is (C).

Question 2

...

Network Theory (2M)

steps to success

GATE AC

In the circuit shown in figure, the switch is closed at time t = 0, while the capacitor is initially charged to -5V [i.e. $V_c(0) = -5V$]



The time after which the voltage across the capacitor becomes zero is (Round off to 3 decimal places) _____ms.

Ans. 0.1386

Sol. Given, initial value of voltage across capacitor

 $V_{C}(0^{-}) = -5 \text{ V}$

When switch is closed and circuit is in steady state (i.e. $t = \infty$, and capacitor becomes open circuit) So circuit becomes as,



Apply KCL at node $V_C(\infty)$ is,

$$\frac{V_{C}(\infty)}{250} + \frac{V_{C}(\infty) - 5}{250} + \frac{V_{R}}{500} = 0 \qquad (\because V_{R} = V_{C}(\infty))$$
$$\frac{V_{C}(\infty)}{250} + \frac{V_{C}(\infty) - 5}{250} + \frac{5 - V_{C}(\infty)}{500} = 0$$
$$2V_{C}(\infty) + 2V_{C}(\infty) - 10 + 5 - V_{C}(\infty) = 0$$
$$3V_{C}(\infty) = 5$$

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052



© Copyright

www. Macebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering







Hence, the correct answer of t is 0.1386 msec.

Question 3

Consider the circuit with an ideal Op-Amp shown in figure,



Analog Electronics (1M)



(A)
$$V_{IN} = V_{REF}$$
 (B) $V_{IN} = 0.5V_{REF}$ (C) $V_{IN} = 2V_{REF}$ (D) $V_{IN} = 2 + V_{REF}$

Ans. A

Sol. Given circuit is shown below,



According to question, $|V_{\rm IN}| << |V_{\rm CC}|$ and $|V_{\rm REF}| << |V_{\rm CC}|$

Here, Op-Amp is ideal and -ve feedback is present so virtual ground concept is applicable. So, $V_+ = V_- = 0$

Thus applying KCL at node N,

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. facebook.com/gateacademy



GATE ACADEMY steps to success...

$$\frac{0 - V_{IN}}{R} + \frac{0 + V_{REF}}{R} + \frac{0 - V_{out}}{R_F} = 0$$
$$\frac{V_{out}}{R_F} = \frac{V_{REF} - V_{IN}}{R}$$
$$V_{out} = \frac{R_F}{R} [V_{REF} - V_{IN}]$$

According to question, $V_{out} = 0$

$$0 = \frac{R_F}{R} \left[V_{REF} - V_{IN} \right]$$
$$V_{REF} - V_{IN} = 0$$
$$V_{REF} = V_{IN}$$

Hence, the correct answer is option (A).

Question 4

A circuit with an ideal OPAMP is shown in the figure. A pulse V_{IN} of 20 ms duration is applied to the input. The capacitors are initially uncharged.



Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

Analog Electronics (2M)

www. **F**acebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering







According to transient theory, at $t = 0^+$, capacitor will be short circuit, so above circuit becomes as,



From above circuit it is clear that,

 $V_{-} \neq V_{+}$

$$V_{-} = V_{IN} = +5 \text{ V}$$
$$V_{+} = 0 \text{ V}$$

Here,

It means, voltage at both terminals of op-amp are unequal and fixed so virtual ground concept is not valid here and op-amp work as a comparator.

Thus, $V_- > V_+$

So,
$$V_{out} = -V_{sat}$$

$$V_{out} = -12 \,\mathrm{V}$$

Hence, the output voltage V_{out} of this circuit at $t = 0^+$ is -12 V.

Question 5

Analog Electronics (1M)

For the circuit with an ideal Op-Amp shown in the figure. V_{REF} is fixed.





V

 \mathbf{V}

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



GATE ACADEMY

$$\frac{\frac{V_{ref}}{2} - V_{in}}{R_{in}} + \frac{\frac{V_{ref}}{2} - V_{out}}{R_{F}} = 0$$

$$\frac{V_{ref}}{2} \left[\frac{1}{R_{in}} + \frac{1}{R_{F}} \right] - \frac{V_{in}}{R_{in}} = \frac{V_{out}}{R_{F}}$$

$$\frac{V_{ref}}{2} \left[\frac{R_{in} + R_{F}}{R_{in} R_{F}} \right] - \frac{V_{in}}{R_{in}} = \frac{V_{out}}{R_{F}}$$

$$\frac{V_{ref}}{2} \left[1 + \frac{R_{F}}{R_{in}} \right] - \left(\frac{R_{F}}{R_{in}} \right) V_{in} = V_{out} \qquad \dots (i)$$

Condition 1 : If $V_{out} = 1$ V when $V_{in} = 0.1$ V then equation (i) becomes as

$$\frac{V_{ref}}{2} \left[1 + \frac{R_F}{R_{in}} \right] - (0.1) \left(\frac{R_F}{R_{in}} \right) = 1 \qquad \dots (ii)$$

Condition 2 : If $V_{out} = 6$ V when $V_{in} = 1$ V then equation (ii) becomes as

$$\frac{V_{ref}}{2} \left[1 + \frac{R_F}{R_{in}} \right] - (1) \left(\frac{R_F}{R_{in}} \right) = 6 \qquad \dots (iii)$$
Assume $\frac{V_{ref}}{2} \left[1 + \frac{R_F}{R_{in}} \right] = x$, then subtracting equation (iii) from (ii) then,
 $\left(x - 0.1 \frac{R_F}{R_{in}} \right) - \left(x - 1 \frac{R_F}{R_{in}} \right) = 1 - 6$

$$0.9 \frac{R_F}{R_{in}} = -5$$

$$\frac{R_F}{R_{in}} = -\frac{5}{0.9} = -5.55$$

Note : As per the given data of question we get negative answer so none of the option is matched.

Electronic Devices (1M)

Question 6

The energy band diagram of a *p*-type semiconductor bar of length *L* under equilibrium condition (i.e. the Fermi energy levels E_F is constant) is shown in the figure. The valance band E_V is sloped since doping is non-uniform along the bar. The difference between the energy levels of the valance band at the two edges of the bar is Δ .



exposed to light such that electron-hole pairs are generated throughout the volume of the bar at the rate of 10^{20} cm⁻³ s⁻¹. If the recombination lifetime is 100 µs and intrinsic carrier concentration of silicon is 10^{10}

www. facebook.com/gateacademy





GATE 2021 [Afternoon Session] Electronics & Communication Engineering





$$X_{n}.N_{D} = X_{p}.N_{A}$$

$$X_{n}.N_{D} = (W - X_{n})N_{A}$$

$$X_{n}(N_{D} + N_{A}) = W.N_{A}$$

$$X_{n} = \frac{WN_{A}}{N_{A} + N_{D}} = \frac{W \times 5 \times 10^{16}}{(5 \times 10^{16}) + (10 \times 10^{16})}$$

$$X_{n} = \frac{W \times (5 \times 10^{16})}{15 \times 10^{16}} = \frac{W}{3}$$
So, $X_{p} = W - X_{n} = W - \frac{W}{3}$

$$X_{p} = \frac{2}{3} W$$

Suppose when N-is depleted completely, during reverse bias so,

...

$$W = 3X_n = 0.6 \ \mu m$$

 $X_n = 0.2 \ \mu m$

$$X_p = \frac{2}{3} \times W = \frac{1.2}{3} = 0.4 \ \mu m$$

i.e. when N is depleted completely (i.e. 0.2 μ m) then and only then *P* side is depleted only by 0.4 μ m only. Thus

$$\begin{cases} X_n = 0.2 \ \mu m \\ W = 0.6 \ \mu m \end{cases} \rightarrow (N \text{ region depleted completely})$$

So, total depletion width (W) under reverse bias is,

$$W = \sqrt{\frac{2\varepsilon(V_0 + V_R)}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)}$$

$$W^2 = \frac{2\varepsilon(V_0 + V_R)}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) = 2004$$

$$(0.6 \times 10^{-6} \times 100)^2 = \frac{2 \times 12 \times 8.85 \times 10^{-14}}{1.6 \times 10^{-19}} \left(\frac{1}{5 \times 10^{16}} + \frac{1}{10 \times 10^{16}}\right) (V_0 + V_R)$$

$$(0.6 \times 10^{-4})^2 = 3.9825 \times 10^{-10} (V_0 + V_R)$$

$$V_0 + V_R = 9.0395$$

$$V_R = 9.0395 - V_0$$

$$V_R = 9.0395 - 0.8$$

 $V_{R} = 8.2395 \text{ V} \approx 8.24 \text{ V}$

Thus, the magnitude of reverse bias voltage that would completely deplete N region is 8.24 V. Hence, the correct answer for V_R is 8.24 V.

Question 9

Control Systems (2M)

steps to success

GATE A

The electrical system shown in figure, converts input source current $i_s(t)$ to output voltage $V_0(t)$.



Current $i_L(t)$ in the inductor and voltage $V_C(t)$ across the capacitor are taken as the state variables, both assumed to be initially equal to zero i.e. $i_L(0) = 0$ and $V_C(0) = 0$. The system is

(A) Completely state controllable as well as completely observable.

- (B) Completely state controllable but not observable.
- (C) Completely state observable but not state controllable.
- (D) Neither state controllable nor observable.

Ans.

Sol. Given circuit is shown below,



GATE 2021 [Afternoon Session] Electronics & Communication Engineering

steps to success...

$$i_{1}(i) = \frac{d}{dt}V_{c}(t) + \frac{V_{c}(t)}{1}$$

$$u = \frac{d}{dt}x_{2} + x_{2}$$

$$u = \dot{x}_{2} + x_{2}$$

$$\dot{x}_{2} = -x_{2} + u \qquad \dots(i)$$
KVL in the loop between inductor and resistor,
$$i_{1}(t) - i_{L}(t) = \frac{d}{dt}i_{L}(t)$$

$$u - x_{1} = \frac{d}{dt}x_{3}$$

$$u - x_{1} = \dot{x}_{1}$$

$$u - x_{1} = \dot{x}_{2}$$

$$u - \dot{x}_{2}$$

$$u - \dot{x}_{1} = \dot{x}_{2}$$

$$u - \dot{x}_{2}$$

© Copyright

www.gateacademy.co.in www. Macebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

<u>∧</u>®

Electromagnetic Theory (2M)

$$A^{T}C^{T} = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ -1 \end{bmatrix}$$

7

Condition of observability,

$$[Q_0] = \begin{bmatrix} C^T & A^T C^T \\ [Q_0] = \begin{bmatrix} 0 & 0 \\ 1 & -1 \end{bmatrix}$$
$$|Q_0| = 0$$

Thus, system is un-observable.

So, the system is neither controllable nor observable.

Hence, the correct option is (D).

Question 10

An antenna with a directive gain of 6 dB is radiating a total power of 16 kW. The amplitude of electric field in free space at a distance of 8 km from the antenna in the direction of 6 dB gain is (Round off to 3

decimal places) _____ V/m.

Ans. 0.2443

Sol. Given : Directive gain
$$G_d(\theta, \phi) = \frac{6}{6} dE$$

Radiation power $P_{rad} = 16 \, \text{kW}$

Distance r = 8 km

Directive gain $G_d(dB) = 6 = 10 \log G_d$

$$G_d = 10^{0.6} = 3.981$$

So maximum electric field amplitude in free space at distance r from antenna is,

$$\left|E_{s}\right|_{\max} = \eta \left[\frac{G_{d} P_{rad}}{2\pi r^{2}}\right] = \frac{120\pi \times 3.981 \times 16 \times 10^{3}}{2\pi (8 \times 10^{3})^{2}} = 0.2443 \,\text{V/m}$$

Hence, the correct answer for $|E_s|_{\text{max}}$ is 0.2443 V/m.

Question 11

Electromagnetic Theory (2M)

For a vector field $\vec{\mathbf{D}} = \rho \cos^2 \phi \hat{\mathbf{a}}_{\rho} + z^2 \sin^2 \phi \hat{\mathbf{a}}_{\phi}$ in a cylindrical coordinate system (ρ, ϕ, z) with unit vector $\hat{a}_{\rho}, \hat{a}_{\phi}$ and \hat{a}_z , the net flux of $\vec{\mathbf{D}}$ leaving the closed surface of the cylinder $(\rho = 3, 0 \le z \le 2)$ (Round off to 2 decimal places) is _____.

Ans. 56.548

Sol. Given : $\vec{\mathbf{D}} = \rho \cos^2 \phi \hat{\mathbf{a}}_{0} + z^2 \sin^2 \phi \hat{\mathbf{a}}_{0}$

Cylinder ($\rho = 3, 0 \le z \le 2$) is shown below,

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. 🖬 acebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering







From this given cylinder,

 $\rho = 3 \text{ m}, z = 0 \text{ to } 2 \text{ m}, \phi = 0 \text{ to } 2\pi$

Shaded portion shows closed surface of cylinder and unit vector that is perpendicular this surface is \hat{a}_{p} thus, net flux (ψ) leaving the closed surface of cylinder is

$$\Psi = \iint \overrightarrow{\mathbf{D}}.\overrightarrow{d\mathbf{s}} = \int_{\phi=0}^{2\pi} \int_{z=0}^{2} (\rho \cos^{2} \phi \ \widehat{\mathbf{a}}_{\rho} + z^{2} \sin^{2} \phi \ \widehat{\mathbf{a}}_{\phi}) \cdot (\rho d\phi dz \ \widehat{\mathbf{a}}_{\rho})$$

$$\Psi = \int_{\phi=0}^{2\pi} \int_{z=0}^{2} \rho^{2} \cos^{2} \phi d\phi dz \bigg|_{\rho=3} \qquad (\because \widehat{a}_{\rho}.\widehat{a}_{\rho} = 1 \text{ and } \widehat{a}_{\rho}.\widehat{a}_{\phi} = 0)$$

$$\Psi = 3^{2} \times (2-0) \times \frac{2\pi}{2} = 18\pi \text{ C}$$

$$\Psi = 18\pi = 56.548 \text{ C}$$
Hence, total flux Ψ living closed surface of the given cylinder as 56.548 C.

Question 12

Electromagnetic Theory (1M)

The vector function $\mathbf{F}(\mathbf{r}) = -x\hat{i} + y\hat{j}$ is defined over a circular are C shown in the figure,





Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

www. Facebook.com/gateacademy

PAGE 18	GATE 2021 [Afternoon Session] Electronics & Communication Engineering GATE ACADEMY steps to success
Ans. Sol.	Consider the vector field $\overline{\mathbf{F}} = \hat{\mathbf{a}}_x (4y - c_1 z) + \hat{\mathbf{a}}_y (4x + 2z) + \hat{\mathbf{a}}_z (2y + z)$ in a rectangular coordinate system (x, y, z) with unit vectors $\hat{\mathbf{a}}_x, \hat{\mathbf{a}}_y, \hat{\mathbf{a}}_z$. If the field \mathbf{F} is irrotational (conservative), then the constant c_1 (in integer) is 0 Given : $\overline{\mathbf{F}} = \hat{\mathbf{a}}_x (4y - c_1 z) + \hat{\mathbf{a}}_y (4x + 2z) + \hat{\mathbf{a}}_z (2y + z)$ Here, $F_x = 4y - c_1 z$, $F_y = 4x - 2z$, $F_z = 2y + z$, For a vector field to be irrotational its curl must be zero, i.e. $\nabla \times \overline{F} = 0$ $\begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ F_x & F_y & F_z \end{vmatrix} = 0$ $\begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ - F_x & F_y & F_z \end{vmatrix} = 0$
	$\begin{vmatrix} \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ 4y - c_1 z & 4x + 2z & 2y + z \end{vmatrix} = 0$ $\hat{a}_x [2 - 2] - \hat{a}_y [0 + c_1] + \hat{a}_z [4 - 4] = 0$ $0 \hat{a}_x - c_1 \hat{a}_y + 0 \hat{a}_z = 0$ $-c_1 \hat{a}_y = 0$ It shows $\hat{a}_y \neq 0$ because it is unit vector.
	Thus, $c_1 = 0$ then the above equation will be satisfied.
Quest	Hence, the correct answer is zero. ion 14 Electromagnetic Theory (1M) The refractive indices of the core and cladding of an optical fiber are 1.50 and 1.48 respectively. The critical propagation angle, which is defined as the maximum angle that the light beam makes with the axis of the optical fiber to achieve the total internal reflection (round off to two decimal places) is degree.
Ans.	9.32
Sol.	Given : Refractive index of core $n_1 = 1.50$ Refractive index of cladding $n_2 = 1.48$ According to the definition of critical propagation angle given in statement of question, θ_1 , which is made with optical fiber axis and leads total internal reflection (TIR) in optical fiber cable, so we can calculate θ_1 as,

www.gateacademy.co.in Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 © Copyright Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052 www. **ff**acebook.com/gateacademy



 Branch Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176
 www.gateacademy.co.in

 Branch Office : Raipur () : 79743-90037, Bhopal () : 89591-87052
 www.facebook.com/gateacademy

PAGE **GATE 2021** [Afternoon Session] 20 Electronics & Communication Engineering

GATE ACADEN steps to succes

Consider a rectangular coordinate system (x, y, z) with unit vector $\mathbf{a}_x, \mathbf{a}_y$ and \mathbf{a}_z . A plane wave travelling in the region $z \ge 0$ with electric field vector $\mathbf{E} = 10\cos(2\times10^8 t + \beta z)\hat{\mathbf{a}}_y$ is incident normally on the plane at z = 0, where β is the phase constant. The region $z \ge 0$ is in free space and the region z < 0 is filled with a lossless medium (permittivity $\varepsilon = \varepsilon_0$ permeability $\mu = 4\mu_0$, where $\varepsilon_0 = 8.85 \times 10^{-12}$ F/m and $\mu_0 = 4\pi \times 10^{-7}$ H/m). The value of reflection coefficient is



© Copyright

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

GATE ACADEN steps to succes

$$\Gamma = \frac{\sqrt{\mu_2} - \sqrt{\mu_1}}{\sqrt{\mu_2} + \sqrt{\mu_1}}$$
$$\Gamma = \frac{\sqrt{4\mu_0} - \sqrt{\mu_0}}{\sqrt{4\mu_0} + \sqrt{\mu_0}}$$
$$\Gamma = \frac{\sqrt{4} - \sqrt{1}}{\sqrt{4} + \sqrt{1}} = \frac{1}{3}$$

Hence, the correct option is (A).

Question 16

Electromagnetic Theory (1M)

The impedance matching network shown in the figure is to match a lossless line having characteristic impedance $Z_0 = 50 \ \Omega$ with a load impedance Z_L . A quarter-wave line having a characteristic impedance $Z_1 = 75 \ \Omega$ is connected to Z_L . Two stubs having characteristic impedance of 75 Ω each are connected to this quarter-wave line. One is a short-circuited (S.C.) stub of length 0.25 λ connected across PS and the other one is an open-circuited (O.C.) stub of length 0.5 λ connected across QR.



Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052

www. facebook.com/gateacademy



GATE 2021 [Afternoon Session] <u>Electronics & Communication Engineering</u>



HAI

steps to success.



GATE 2021 [Afternoon Session] <u>Electronics & Communication Engineering</u>

$$Z_{PS} = \frac{75^2}{Z_L} || \infty = \left(\frac{75^2}{Z_L}\right)$$

Now Transmission Line arrangement becomes as-

Main transmission line

$$Z_0 = 50 \ \Omega \qquad \qquad \bigotimes Z_{PS} = \frac{75^2}{Z_L}$$

GATE AC

steps to succe

Hence Z_{PS} work as load for main Transmission line.

For matching of main Transmission line with load (Z_{PS}) ,

$$Z_{PS} = Z_o$$
$$\frac{75^2}{Z_L} = 50 \Longrightarrow Z_L = \frac{75^2}{50} = 112.5\Omega$$

Hence, the correct option is (A)

Method 2 :

From given arrangement, it is clear that,

$$Z_{in}\left[l = \frac{\lambda}{2}\right]_{Line-1} = \left(Z_{L}\right)_{Line-1} = \infty$$
$$Z_{in}\left[l = \frac{\lambda}{4}\right]_{Line-3} = \frac{Z_{0}^{2}}{\left(Z_{L}\right)_{Line-3}} = \frac{Z_{0}^{2}}{0} = \infty$$

So, input impedance of both line-1 and line-3 are ∞ (i.e. open circuit) so it does not make any effect on main transmission line, so given transmission line configuration becomes as,



Thus Input Impedance at terminal PS is,

$$(Z_{in})_{PS} = \frac{Z_0^2}{Z_L} = \frac{75^2}{Z_L} \Omega$$

So $(Z_{in})_{PS}$ work as load for main transmission line so arrangement of transmission line becomes as,

© Copyright

PAGE GATE 2021 [Afternoon Session] 24 Electronics & Communication Engineering







Hence $(Z_{in})_{PS}$ work as load for main Transmission line so the condition, for matching the main Transmission line with load $(Z_{in})_{PS}$ is

$$(Z_{in})_{PS} = Z_0$$

 $\frac{75^2}{Z_L} = 50$
 $Z_L = \frac{75^2}{50} = 112.5\Omega$

Hence, the correct option is (A)

Question 17

Consider the circuit shown in figure.

 $\begin{array}{c} 3\Omega \mu^{\mu} \\ 7\Omega \\ P \\ & &$

Network Theory (1M)

The current I flowing through the 7Ω resistor between P and Q (Round off to 1 decimal places) is

Ans. 0.5

Re-arrange the above circuit as shown below,

www.gateacademy.co.in www.facebook.com/gateacademy



Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🚫 : 89591-87052

www. Macebook.com/gateacademy





Thus, analog output from 8 bit unipolar DAC is,

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success.

Digital Electronics (2M)

GATE AC



$$V_{\text{out}} = \left(\frac{V_{FS}}{2^n - 1}\right) \times 150 = \left(\frac{7.68}{2^8 - 1}\right) \times 150 = 4.517 \text{ Volt}$$

(B) 5 ns

Hence, the analog output voltage of the 8 bit unipolar DAC is 4.517 Volt

Question 20

The propagation delays of the XOR gate, AND gate and multiplexer (MUX) in the circuit shown in the figure are 4 ns, 2 ns and 1 ns, respectively.



If all the inputs P, Q, R, S and T are applied simultaneously and held constant, the maximum propagation delay of the circuit is

(A) 3 ns

(C) 6 ns

(D) 7 ns

Ans.

Sol. Given :

С

Delay of XOR gate = 4ns Delay of AND gate = 2ns Delay of MUX = 1ns

Case 1 :

Assuming T = 0 then selection line of MUX $S_0 = 0$, so that MUX input '0' get enable so path followed by signal in the given circuit is shown by dotted lines as,





steps to succ

So total propagation delay τ_1 from input to output is,

 $\tau_1 = (Propagation delay of AND gate) + (Propagation delay of MUX-2)$

 $\tau_1 = 2ns + 1ns = 3ns$

Hence MUX input '0' get enable then propagation delay of given circuit $\tau_1 = 3ns$

Case 2 :

Assuming T = 1 then selection line of MUX is $S_0 = 1$, so that MUX input '1' get enable so path followed by signal in the given circuit is shown by dotted lines as,



So total propagation delay τ_2 from input to output is,

 $\tau_2 = (Propagation delay of AND gate) + (Propagation delay of MUX-1) +$

(Propagation delay of AND gate) + (Propagation delay of MUX-2)

 $\tau_2 = 2ns + 1ns + 2ns + 1ns = 6ns$

Hence MUX input '1' get enable then propagation delay of given circuit $\tau_2 = 6ns$

Hence maximum delay of circuit is MAX $(\tau_1, \tau_2) = MAX(3ns, 6ns) = 6 ns$

Hence, the correct option is (C).

Question 21

Digital Electronics (2M)

The propagation delay of the exclusive-OR (XOR) gate in the circuit is 3 ns. The propagation delay of all the flip-flops is assumed to be zero. The clock (Clk) frequency provided to the circuit is 500 MHz.



www. Macebook.com/gateacademy



The minimum number of triggering clock edges after which the flip-flop output $Q_2 Q_1 Q_0$ becomes 100 is 5.

Question 22

Network Theory (2M)

The switch in the circuit in the figure is in position P for a long time and then moved to position Q at time t=0.



GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success.

GATE ACA

Switch is at position P, inductor behaves as short circuit and capacitor behaves as open circuit. So circuit becomes as,

$$5k\Omega - p - 5k\Omega$$

$$20 \vee \bigoplus 20k\Omega - V(0^{-}) = V_{c}(0^{-})$$

$$i_{L}(0^{-})$$
Apply KVL in loop shown by dotted line,
$$20 - 5 \times i_{L}(0^{-}) - 5 \times i_{L}(0^{-}) - 10 \times i_{L}(0^{-}) = 0$$

$$i_{L}(0^{-}) = \frac{20}{5 + 5 + 10}$$

$$i_{L}(0^{-}) = 1mA$$
So voltage $V_{c}(0^{-})$ is
$$V_{c}(0^{-}) = 10 \times i_{L}(0^{-})$$

$$V_{c}(0^{-}) = 10 \times 1$$

$$V_{c}(0^{-}) = 10 \vee 1$$
Thus current and voltage across inductor and capacitor at $t = 0^{+}$ is,
$$i_{L}(0^{-}) = i_{L}(0^{+}) = 1mA$$

$$V_{c}(0^{-}) = V_{c}(0^{+}) = 10 \vee 1$$

(ii) At $t = 0^+$:

Switch is at position Q and Inductor is replaced by a current source with initial value $i_L(0^+)$ and capacitor is replaced by voltage source with initial value $V_C(0^+)$ so circuit becomes as,



Apply nodal analysis at node A,

$$\frac{10}{5} + i_C(0^+) + 1 = 0$$
$$2 + i_C(0^+) + 1 = 0$$

© Copyright

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

GATE 2021 [Afternoon Session] **Electronics & Communication Engineering**

Computer Organization (2M)

 $i_{C}(0^{+}) = -3 \,\mathrm{mA}$

So voltage across capacitor at $t = 0^+$ is,

$$i_{C}(0^{+}) = C \frac{d}{dt} V_{C}(0^{+})$$
$$\frac{d}{dt} V_{C}(0^{+}) = \frac{i_{C}(0^{+})}{C} = \frac{-3}{1} = -3 \text{ V/sec}$$

Hence, the correct option is (C).

Question 23

The content of the registers are $R_1 = 25$ H, $R_2 = 30$ H and $R_3 = 40$ H. The following machine instructions are executed

- PUSH $\{R_1\}$
- PUSH $\{R_2\}$
- PUSH $\{R_3\}$
- POP $\{R_1\}$
- POP $\{R_2\}$
- POP $\{R_3\}$

After execution, the content of registers R_1, R_2, R_3 are

- (A) $R_1 = 40$ H, $R_2 = 30$ H, $R_3 = 25$ H
- (B) $R_1 = 25 \text{ H}, R_2 = 30 \text{ H}, R_3 = 40 \text{ H}$
- (C) $R_1 = 30 \text{ H}$, $R_2 = 40 \text{ H}$, $R_3 = 25 \text{ H}$ (D) $R_1 = 40 \text{ H}$, $R_2 = 25 \text{ H}$, $R_3 = 30 \text{ H}$

Ans. Α

© Copyright

```
Given : R_1 = 25 \text{ H}, R_2 = 30 \text{ H}, R_3 = 40 \text{ H}
Sol.
```

PUSH
$$\{R_1\}$$

PUSH $\{R_2\}$ Since 2004

PUSH $\{R_3\}$

- POP $\{R_1\}$
- POP $\{R_2\}$
- POP $\{R_3\}$

www.gateacademy.co.in www. facebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering







Hence, $R_1 = 40 \text{ H}$, $R_2 = 30 \text{ H}$, $R_3 = 25 \text{ H}$

Hence, the correct option is (A).

Question 24

The exponential Fourier series representation of continuous time periodic signal x(t) is defined as

$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}$$

where ω_0 is the fundamental angular frequency of x(t) and the coefficient of series are a_k .

The following information is given about x(t) and a_k .

(i) x(t) is real and even having fundamental period of 6 sec.

(ii) Average value of x(t) is 2.

(iii)
$$a_k = \begin{cases} k, & 1 \le k \le 3\\ 0, & k > 3 \end{cases}$$

The average power of the signal x(t) (round of one decimal place) is _____

Ans. 32

Sol. Given :

$$x(t) = \sum_{k=\infty}^{\infty} a_k e^{jk\omega_0 t}$$
 Since 2004

- (i) x(t) is real and even with T = 6 sec
- (ii) Average value of x(t)=2

(iii)
$$a_k = \begin{cases} k, & 1 \le k \le 3 \\ 0, & k > 3 \end{cases} \Rightarrow a_k = \{\dots, 1, 2, 3\}$$

From symmetry conditions, as x(t) is real and even, so its fourier series coefficients will also be real and even.

i.e. $a_k^* = a_k$ and $a_{-k} = a_k$

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. 🖬 acebook.com/gateacademy

Signals & Systems (2M)





so if
$$a_1 = 1 \Longrightarrow a_{-1} = a_1 = 1$$

 $a_2 = 2 \Longrightarrow a_{-2} = a_2 = 2$
 $a_3 = 3 \Longrightarrow a_{-3} = a_3 = 3$
 $a_k = 0$ for $k > 3$
 $a_{-k} = 0$ for $k < -3$

Also, given that average value of x(t)

i.e. $\frac{1}{T} \int_{0}^{T} x(t) dt = a_0 = 2$

So, the complete set of Fourier series coefficients is given as

$$a_x = \{3, 2, 1, 2, 1, 2, 3\} = \{a_{-3}, a_{-2}, a_{-1}, a_0, a_1, a_2, a_3\}$$

Using Parseval's theorem, average power of x(t) is given as

$$P_{x} = \frac{1}{T} \int_{0}^{T} |x(t)|^{2} dt = \sum_{k=-\infty}^{\infty} |a_{k}|^{2}$$

$$P_{x} = (3)^{2} + (2)^{2} + (1)^{2} + (2)^{2} + (1)^{2} + (2)^{2} + (3)^{2}$$

$$P_{x} = 9 + 4 + 1 + 4 + 1 + 4 + 9$$

$$P_{x} = 32 \text{ W}$$

Hence, the average power of signal x(t) is 32 W

Question 25

Ans. Sol.

Signals & Systems (1M)

Consider a real-valued base-band signal x(t), band limited to 10 kHz. The Nyquist rate for the signal

$$y(t) = x(t) \cdot x \left(1 + \frac{t}{2}\right) \text{ is }$$
(A) 15 kHz (B) 30 kHz (C) 60 kHz (D) 20 kHz

B

Given :

$$x(t) \text{ is band limited to 10 kHz}$$

$$y(t) = x(t) \cdot x \left(1 + \frac{t}{2}\right) = x(t) \cdot x \left[\frac{1}{2}(t+2)\right]$$

Method 1 :

Assuming magnitude spectrum of x(t) is shown below,





 $\blacktriangleright f(kHz)$

|X(f)|

Δ

10



Let

$$x(t) \xleftarrow{\text{F.T.}} X(f)$$

$$x_1(t) = x(t+1) \xleftarrow{\text{F.T.}} e^{j2\pi f} X(f) = X_1(f)$$

 $x(t) \xleftarrow{\text{F.T}} -$

Magnitude spectrum of $x_1(t)$,

$$|X_{1}(f)| = |X(f)|$$

$$|X_{1}(f)| = |X(f)|$$

$$|X_{1}(f)| = |X(f)|$$

$$x_{1}(t) \xleftarrow{\text{FT}} \xrightarrow{-10 \quad 0 \quad 10} f(\text{kHz})$$

$$x_{2}(t) = x_{1}\left(\frac{t}{2}\right) = x\left(\frac{t}{2}+1\right) \xleftarrow{\text{FT}} 2e^{j2\pi f} X(2f) = X_{2}(f)$$

Magnitude spectrum of $x_2(t)$,

$$|X_2(f)| = 2|X(2f)|$$

$$x_2(t) = x \left(1 + \frac{t}{2}\right) \xleftarrow{\text{F.T}} \underbrace{-5 \quad 0 \quad 5}_{-5 \quad 0 \quad 5} f(\text{kHz})$$

Thus applying the property of convolution,

$$y(t) = x(t) \cdot x_{2}(t) \xleftarrow{\text{F.T.}} Y(f) = X(f) \otimes X_{2}(f)$$

$$y(t) = x(t) \cdot x_{2}(t) \xleftarrow{\text{F.T.}} \frac{|X(f)|}{-10 \ 0 \ 10} f(\text{kHz}) \xrightarrow{-5 \ 0 \ 5} f(\text{kHz})$$

So that spercturm of Y(*f*) is shown below,


So, the nyquist rate of y(t) = 15 kHzHence, the correct option is (B).

Method 2 :

Given: $y(t) = x(t) \cdot x\left(1 + \frac{t}{2}\right)$

Where maximum frequency component of x(t) is $f_{m_1} = 10$ kHz

To find Nyquist rate of sampling for y(t) we need to find maximum frequency component in y(t)As y(t) is obtained by multiplication of two functions in time domain so Fourier transform of y(t), i.e. $Y(\omega)$ will be the convolution of individual transforms of multiplied signals.

Let,

$$x\left(\frac{t}{2}+1\right) = x_{1}(t)$$

$$y(t) = x(t).x_{1}(t)$$

$$Y(\omega) = \frac{1}{2\pi}X(\omega) \cdot X_{1}(\omega) = X(f) \cdot X_{1}(f) \qquad \dots (i)$$

When two functions are convolved, then the left and right most limits of existence of resultant function will be addition of left and right most frequencies of X(f) and $X_1(f)$

Given, X(f) has maximum frequency of 10 kHz

$$x(t) \rightarrow f_{m_1} = 10 \,\mathrm{kHz}$$

As time shifting do not have any effect on the existence duration of its spectrum

So

$$x(t+1) \rightarrow f'_m = 10 \,\mathrm{kHz}$$

As expansion in time domain results in compression in frequency domain, so after applying time scaling

$$x\left(\frac{t}{2}+1\right) \rightarrow f_{m_2} = \frac{10}{2} = 5 \,\mathrm{kHz}$$

So, the maximum frequency component in the convolved signal y(t) is

$$f_m = f_{m1} + f_{m2} = 15 \text{ kHz}$$

So, the Nyquist sampling rate is given by,

$$f_s = 2f_m = 2 \times 15 \text{ kHz} = 30 \text{ kHz}$$

 Branch Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176
 www.gateacademy.co.in

 Branch Office : Raipur S : 79743-90037, Bhopal S : 89591-87052
 www.flacebook.com/gateacademy



Signals & Systems (2M)

GATE ACAD

For a unit step input
$$u[n]$$
, a discrete time LTI system produces an output signal
 $\left[2\delta[n+1]+\delta[n]+\delta[n-1]\right]$. Let $y[n]$ be the output of system for an input $\left[\left(\frac{1}{2}\right)^n u[n]\right]$. The value of
 $y[0]$ is ______.
Ans. **0**
Sol. Given response of the system for step input, i.e. step response is,
 $S[n] = 2\delta[n+1]+\delta[n]+\delta[n-1]$
Impulse response of the system can be obtained by taking first difference of $S[n]$
 $h[n] = S[n] - S[n-1]$
 $h[n] = 2\delta[n+1] + \delta[n] + \delta[n-1] - 2\delta[n] - \delta[n-1] - \delta[n-2]$
 $h[n] = 2\delta[n+1] - \delta[n] - \delta[n-2]$
 $y[n] = 2\delta[n+1] - \delta[n] - \delta[n-2]$
 $y[n] = 2\delta[n+1] - \delta[n] - \delta[n-2]$
 $y[n] = 2\left(\frac{1}{2}\right)^n u[n] \otimes \{2\delta[n+1] - \delta[n] - \delta[n-2]\}$
 $y[n] = 2\left(\frac{1}{2}\right)^{n+1} u[n+1] - \left(\frac{1}{2}\right)^n u[n] - \left(\frac{1}{2}\right)^{n+2} u[n-2]$ ($\because x[n] \otimes \delta[n-n_0] = x[n-n_0]$)
Substituting $n = 0$ both sides,
 $y[0] = 2\times \left(\frac{1}{2}\right)^1 u[1] - \left(\frac{1}{2}\right)^2 u[2] - \frac{1}{2} u[2] u[2] - \frac{1}{2} u[2] u[2] - \frac{1}{2} u[2] u[2] - \frac{1}{2} u[2] u[2] - \frac{1}{2} u[2] - \frac{1}{$

www.gateacademy.co.in



...(i)

...(iii)

Consider the signal $x[n] = 2^{n-1}u[-n+2]$ and $y[n] = 2^{-n+2}u[n+1]$. Where u[n] is the unit step sequence. Let $X(e^{j\omega})$ and $Y(e^{j\omega})$ be the discrete time Fourier transform of x[n] and y[n] respectively. The value of integral

$$\frac{1}{2\pi}\int_{0}^{2\pi}X(e^{j\omega})Y(e^{-j\omega})d\omega$$

(round off to one decimal places) is

Ans. 8

Sol. Given :
$$x[n] = 2^{n-1}u[-n+2] \xrightarrow{DTFT} X(e^{j\omega})$$

$$y[n] = 2^{-n+2} u[n+1] \xrightarrow{DTFT} Y(e^{j\omega})$$

We have to evaluate the integral,

$$I = \frac{1}{2\pi} \int_{0}^{2\pi} X(e^{j\omega}) Y(e^{-j\omega}) d\omega$$

If $p[n] \leftarrow \overset{\text{DTFT}}{\longrightarrow} P(e^{j\omega})$, then from synthesis equation of DTFT

$$p[n] = \frac{1}{2\pi} \int_{0}^{2\pi} P(e^{j\omega}) e^{j\omega n} d\omega$$
$$p[0] = \frac{1}{2\pi} \int_{0}^{2\pi} P(e^{j\omega}) d\omega \qquad \dots (ii)$$

From equation (i) and (ii),

If
$$P(e^{j\omega}) = X(e^{j\omega})Y(e^{-j\omega})$$
 then, $I = p[0]$

If
$$y[n] \longleftrightarrow Y(e^{j\omega})$$

Applying time reversal property,

$$y[-n] \longleftrightarrow Y(e^{-j\omega})$$

Let y[-n] = z[n], then using convolution property,

$$x[n] \otimes z[n] \longleftrightarrow X(e^{j\omega}) \cdot Y(e^{-j\omega}) = P(e^{j\omega})$$

So,

$$p[n] = x[n] \otimes z[n]$$

Expend convolution as,

$$p[n] = \sum_{k=-\infty}^{\infty} x[k]z[n-k]$$

Here,

$$x[k] = 2^{k-1}u[-k+2]$$

 $x[n] = 2^{n-1}u[-n+2]$

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176

www.gateacademy.co.in www. facebook.com/gateacademy

© Copyright

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

$$z[n] = y[-n] = 2^{n+2}u[-n+1]$$

$$z[n-k] = 2^{n-k+2}u[-n+k+1]$$

...

$$p[n] = \sum_{k=-\infty}^{\infty} 2^{k-1} u[-k+2] \cdot 2^{n-k+2} u[-n+k+1]$$

As required integral, $I = p[n]|_{n=0} = p[0]$

$$p[0] = \sum_{k=-\infty}^{\infty} 2^{k-1} u[-k+2] \cdot 2^{-k+2} u[k+1]$$

Sequence, u[-k+2]=1 only for $-\infty < k < 2$, thus modifying limit of summation

$$p[0] = \sum_{k=-\infty}^{2} 2^{k-1-k+2} \cdot 1 \cdot u[k+1]$$
$$p[0] = \sum_{k=-\infty}^{2} 2u[k+1]$$

Sequence u[k+1] = 1 only for $-1 < k < \infty$, thus modifying lower limit of summation.

$$p[0] = \sum_{k=-1}^{2} 2 \times 1 = 2 \sum_{k=-1}^{2} (1)^{k}$$

$$p[0] = 2[1+1+1+1] = 8$$

$$I = \frac{1}{2\pi} \int_{0}^{2\pi} X(e^{j\omega}) \cdot Y(e^{-j\omega}) d\omega = \frac{1}{2\pi} \int_{0}^{2\pi} P(e^{j\omega}) d\omega$$

$$I = p[0] = 8$$

So,

Hence, the value of given integral is 8.

Question 28

Signals & Systems (1M)

Consider two 16 point sequences x[n] and h[n]. Let the linear convolution x[n] and h[n] be denoted by y[n], while z[n] denotes the 16 point inverse discrete Fourier transform (IDFT) of the product of the 16 point DFTs of x[n] and h[n]. The value(s) of k for which z[k] = y[k] is/are

(A)
$$k = 0, 1, 2, \dots, 15$$
 (B) $k = 0$ (C) $k = 15$ (D) $k = 0$ or 15

Ans. C

Sol.

Given :
$$x[n]$$
 and $h[n]$ are 16 point sequences

and
$$y[n] = x[n] \otimes h[n]$$
 ...(i)
Also, $z[n] = IDFT[X(k) \cdot H(k)]$
Where, $x[n] \xleftarrow{DFT}{16point} X(k)$

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. 🖬 acebook.com/gateacademy



GATE AC

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

$$h[n] \xleftarrow{DFT}{16 \text{ point}} H(k)$$

From circular convolution property of DFT.

$$x[n] (N) h[n] \xleftarrow{DFT} X(k) \cdot H(k)$$
$$z[n] = x[n] (N) h[n]$$

So,

We have to find value of k , for which y(k) = z(k).

i.e., value of n, for which linear and circular convolutions of 16 point sequences x[n] and h[n] are same.

GATE ACA

...(ii)

steps to success

From definitions of linear convolution,

$$y[n] = \sum_{k=-\infty}^{\infty} x[k] \cdot h[n-k]$$

From definitions of circular convolution,

$$z[n] = \sum_{k=0}^{N-1} x(k) \cdot h[(n-k)]_{N} \text{ where, } N = 16$$

Assuming two 16 point sequences as,

$$x[n] = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$$

$$h[n] = \{a, b, c, d, e, f, g, h, i, j, k, l, m, n, o, p\}$$

So, linear convolution y[n] is,

...

From 16 point circular convolution,

$$z[n] = \sum_{K=0}^{15} x(k) \cdot h[(n-k)]_{16}$$
$$z[0] = \sum_{K=0}^{15} x(k) \cdot h[(-k)]_{16}$$

GATE 2021 [Afternoon Session] Electronics & Communication Engineering







Thus,
$$z(0) = (a \times 1) + (b \times 2) + (c \times 3) + (d \times 4) + (e \times 5) + (f \times 6) + (g \times 7)$$

$$(h \times 8) + (i \times 9) + (j \times 10) + (k \times 11) + (l \times 12) + (m \times 13) + (n \times 14)$$

 $+(o \times 15) + (p \times 16) \dots$ (ii)

From equations (i) and (ii), $z(0) \neq y(0)$

So, z(k) = y(k) is not satisfied for k = 0 and hence options (A), (B) and (D) are wrong. Now we are choosing option (C) and verify it as follows,

Linear convolution, $y[n] = \sum_{k=-\infty}^{\infty} x[k] \cdot h[n-k]$

Taking n = 15, $y[15] = \sum_{k=-\infty}^{\infty} x[k] \cdot h[15 - k]$

To find h[15-k], shifting sequence h(-k) 15 times towards right hand side.

...

© Copyri

$$x(k) = \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16\}$$

$$h[-k] = \{p, o, n, m, l, k, j, i, h, g, f, e, d, c, b, a\}$$
$$h[15-k] = \{p, o, n, m, l, k, j, i, h, g, f, e, d, c, b, a\}$$

$$y(15) = p + 2o + 3n + 4m + 5l + 6k + 7j + 8i + 9h + 10g + 11f + 12e$$

$$+13d + 14c + 15b + 16a$$
 ...(iii)

Circular convolution,

$$z[n] = \sum_{k=0}^{15} x(k) \cdot h[(n-k)]_{16}$$
$$z[15] = \sum_{k=0}^{15} x(k) \cdot h[(15-k)]_{16}$$

oht -	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
5111	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. ff acebook.com/gateacademy



© Copyright

www. Macebook.com/gateacademy



GATE ACADEMY steps to success...

(ii)
$$\frac{W}{L} = 10$$

(iii)
$$V_{GS} = 1 \text{ V}$$

Drain to source current (I_{DS}) when N-MOS is saturation is given by,

$$I_{D} = I_{DS} = \frac{\mu_{n}C_{ox}}{2} \times \frac{W}{L} (V_{GS} - V_{T})^{2}$$
 (For NMOS in saturation)

$$I_{D} = I_{DS} = \frac{100 \times 10^{-6}}{2} \times 10(1 - V_{T})^{2}$$

$$I_{D} = \frac{1}{2}(1 - V_{T})^{2}$$

$$V_{DD} = 3 V$$

$$I_{D} = 3 V$$

$$I_{D} = 20 \text{ k}\Omega$$

Apply KVL at outer loop of N-MOS,

$$V_{DS} = 3 - 20 \times I_{DS}$$

Put the value of I_{DS} , in above equation we get

$$V_{DS} = 3 - \frac{20}{2} (1 - V_T)^2$$
$$V_{DS} = 3 - 10 (1 - V_T)^2$$

MOSFET operates in saturation if over drive voltage $V_{DS} \ge V_{OV}$ as shown below,



Copyright Branch Office : Raipur (S. : 79743-90037, Bhopal (S. : 89591-87052)

www. facebook.com/gateacademy





steps to success.

For stability or marginal stability of given system, the coefficient of first column of Routh table should be positive or same sign so,

(i)
$$\frac{18-2K_p}{4} > 0$$

$$K_P < 9$$

Thus, K_p must varies from, $(-1) < K_p < 9$

(ii)
$$\frac{\left(\frac{18-2K_{p}}{4}\right)(2+2K_{p})-8K_{I}}{\frac{18-2K_{p}}{4}} = 0$$
$$2+2K_{p}-\frac{8K_{I}\times4}{18-2K_{p}} = 0$$
$$1+K_{p}=\frac{16K_{I}}{18-2K_{p}}$$
$$1+K_{p}=\frac{8K_{I}}{9-K_{p}}$$
$$K_{I}=\frac{(1+K_{p})(9-K_{p})}{8}$$

Here, K_I is a function of K_P .

For maxima or minima, $\frac{d}{dK_P}K_I = 0$

$$\frac{d}{dK_{p}} \left[\frac{(1+K_{p})(9-K_{p})}{8} \right] = 0$$

$$\frac{1}{8} [(1+K_{p})(-1)+9-K_{p}] = 0$$

$$9-K_{p} = 1+K_{p}$$

$$2K_{p} = 8$$

$$K_{p} = 4$$

$$2004$$

Now, double derivative of K_I is,

$$\frac{d^2}{dK_p^2}K_I = -\frac{1}{4} < 0$$

It means, K_I has maxima at $K_P = 4$.

www.gateacademy.co.in

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success..

GATE AC



Thus, maximum value of K_I at $K_P = 4$ will be,

$$[K_I]_{\text{max}} = \frac{(1+4)(9-4)}{8} = 3.125$$

Question 31

A box contains the following three coins

- (i) A fair coin with head on one face and tail on other face.
- (ii) A coin with heads on both faces.
- (iii) A coin with tail on both faces.

A coin is picked randomly from box and tossed. Out of the two remaining coins in the box, one coin is then picked randomly and tossed. If the first toss result in a head, the probability of getting a head in the second toss is

(A) 2/5 (B) 1/3 (C) 1/2 (D) 2/3

Ans. B

Sol. Method 1 :

There are three types of coins

- (i) Unfair coin with head on both side (*UH*)
- (ii) Unfair coin with tail on both side (UT)



 Image: Copyright
 Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176
 www.gateacademy.co.in

 Branch Office : Raipur \$: 79743-90037, Bhopal \$: 89591-87052
 www.facebook.com/gateacademy

Ans.

Engineering Mathematics (2M)

PAGE 48

GATE 2021 [Afternoon Session] **Electronics & Communication Engineering**





© Copyright

Ans.

Sol.

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

www.gateacademy.co.in www. Macebook.com/gateacademy

Engineering Mathematics (1M)

GATE 2021 [Afternoon Session] Electronics & Communication Engineering

$$\frac{1}{\sqrt{y}}\frac{dy}{dx} + \frac{x}{1 - x^2} \left(\frac{y}{\sqrt{y}}\right) = x$$

Dividing both side with \sqrt{y}

$$y^{-\frac{1}{2}}\frac{dy}{dx} + \frac{x}{1-x^{2}}y.y^{-\frac{1}{2}} = x$$

$$y^{-\frac{1}{2}}\frac{dy}{dx} + \frac{x}{1-x^{2}}y^{\frac{1}{2}} = x$$
 ...(i)

$$y^{\frac{1}{2}} = t$$
 ...(ii)

Let,

Differentiating equation (ii), both side with respect to x,

$$\frac{1}{2}y^{-\frac{1}{2}}\frac{dy}{dx} = \frac{dt}{dx}$$

$$y^{-\frac{1}{2}}\frac{dy}{dx} = 2\frac{dt}{dx}$$
...(iii)

Putting equation (iii) into equation (i),

$$2\frac{dt}{dx} + \frac{x}{1-x^2}t = x$$
$$\frac{dt}{dx} + \frac{1}{2}\left[\frac{x}{(1-x^2)}\right]t = \frac{x}{2}$$
...(iv)

Compare equation (iv) with Labntiz first order differential equation,

$$\frac{dt}{dx} + Pt = Q$$

$$P = \frac{1}{2} \left[\frac{x}{1 - x^2} \right], \quad Q = \frac{x}{2}$$

So,

Integrating factor (I.F) is given by,

I.F =
$$e^{\int Pdx} = e^{\frac{1}{2}\int \frac{x}{1-x^2}dx}$$
 C C 2 0 4
I.F = $e^{-\frac{1}{4}\int \frac{-2x}{1-x^2}dx}$
I.F = $e^{-\frac{1}{4}\log_e(1-x^2)}$
I.F = $e^{\log_e(1-x^2)^{-1/4}}$
I.F = $(1-x^2)^{-\frac{1}{4}}$

Hence, the correct option is (B).

Question 33

Computer Organization (1M)

GATE ACA

steps to success.

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in	
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. f acebook.com/gateacademy	

PAGE 51	GATE 2021 Electronics & Co	[Afternoon Session Communication Engi	on] neering	GATE ACADEMY® steps to success
	Addressing of a 32 K	×16 memory is realized	using a single decoder	The minimum number of AND
	gate required for the de	ecoder is		
	(A) 2^8	(B) 2^{32}	(C) 2^{15}	(D) 2^{19}
Ans.	C			
50 1.	Given : Addressing of memory	$y = 32 \text{ K} \times 16$		
	Addressing of memory	$y = 2^5 \times 2^{10} \times 16$	(:: $K = 2^{10}$)	
	Addressing of memory	$y = 2^{15} \times 16$	R	
	So 32 K×16 memory	needs 15 address lines		
	So it will need decoder	: of size 15×2^{15} , which	will need 2 ¹⁵ AND ga	tes.
	Hence, the correct opti	on is (C).		
Quest	ion 34			Engineering Mathematics (2M)
	A real 2×2 non-singu	lar matrix A with repeate	ed Eigen value is given	1 as
	$A = \begin{bmatrix} x \\ 3 \end{bmatrix}$	$\begin{bmatrix} -3.0 \\ 0 & 4.0 \end{bmatrix}$		
	where x is a real positi	ve number. <mark>Th</mark> e value of	x (round off to one de	cimal place) is
Ans.	10			
Sol.	Given : $A = \begin{bmatrix} x & -3 \\ 3.0 & 4 \end{bmatrix}$	0		
	It is given that Eigen v	alue of matrix <mark>A is</mark> repea	ited	
	Let the repeated Eigen	values are		
	$\lambda_1 = \lambda$		- T-	E .
	$\lambda_2 = \lambda$			
	We know that, sum of	the Eigen value of matri	x [A] is equal to trace	of matrix
	$\lambda_1 + \lambda_2 = \text{Trace} (\lambda_1 + \lambda_2)$	(4) = Sum of diagonal ele	ements of matrix $[A]$)4
	$\lambda + \lambda = x + 4$			
	$2\lambda = x + 4$			
	$\lambda = \frac{\lambda + 1}{2}$		(i)	
	We know that, product	of Eigen value is equal	to determinant of mat	rix $[A]$
	$\lambda_1 \times \lambda_2 = A $			
	$\lambda \times \lambda = 4x + 9$			
	Head Office : A/114	-115, Smriti Nagar, Bhilai (C.O	G.), Contact : 9713113156. 9	589894176 www.gateacademy.co.in

www. facebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success...

	$\lambda^2 = 4x + 9 \qquad \dots (ii)$	
	Putting $\lambda = \frac{x+4}{2}$ into equation (ii)	
	$\left(\frac{x+4}{2}\right)^2 = 4x+9$	
	$x^2 + 8x + 16 = 16x + 36$	
	$x^2 - 8x - 20 = 0$	
	$x^2 - 10x + 2x - 20 = 0$	
	x(x-10) + 2(x-10) = 0	
	(x-10)(x+2) = 0	
	x = 10, x = -2	
	It is given that x is positive real number, therefore we will select $x=10$.	
	Hence, the correct answer is 10.	
Quest	Two continuous random variables V and V are related as	
	Y = 2X + 3	
	Let σ_X^2 , σ_Y^2 denote the variance of X and Y respectively. The variance are related as,	
	(A) $\sigma_Y^2 = 2\sigma_X^2$ (B) $\sigma_Y^2 = 4\sigma_X^2$ (C) $\sigma_Y^2 = 5\sigma_X^2$ (D) $\sigma_Y^2 = 25\sigma_X^2$	
Ans.	В	
Sol.	Given : $\operatorname{Var}[X] = \sigma_X^2$	
	$\operatorname{Var}[Y] = \sigma_Y^2$	
	Y = 2X + 3	
	Taking variance on both sides, Var(Y) = Var[2X+3]	
	$Var(Y) = Var(2X) + Var(3) \qquad \dots (i)$	
	Since, from the property of variance, for any constant "a"	
	$Var[aX] = a^{2}Var[X]$	
	$\operatorname{Var}[a] = 0$	
	So, equation (i) becomes as,	
	$\operatorname{Var}(Y) = 2^2 \operatorname{Var}(X) + 0$	
	$\operatorname{Var}(Y) = 4\operatorname{Var}(X)$	
	$\sigma_Y^2 = 4\sigma_X^2$	
	Hence, the correct option is (B)	
	C Key Point	
0	Head Office : A/114-115, Smrtti Nagar, Bhilai (C.G.), Contact : 9/13113156, 9589894176 WWW.gateacademy.co.	1

© Copyright

Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

www.gateacademy.co.in www. Macebook.com/gateacademy







GATE 2021 [Afternoon Session] PAGE **Electronics & Communication Engineering**

54



GATE A rtebs to succ

Thus we will find residue at pole $x_1 = 0$ and $x_2 = 2i$. Residue of f(x) with multiple pole at x = a with order m is given by, $R(x)\Big|_{x=a} = \frac{1}{(m-1)!} \left| \frac{d^{m-1}}{dx^{m-1}} (x-a)^m f(x) \right|$ Residue at $x_1 = 0$ is given by, $R(x_1) = \frac{1}{(2-1)!} \left| \frac{d}{dx} x^2 \frac{\sin x}{x^2(x+4)} \right|_{a}$ $R(x_1) = \frac{d}{dx} \left| \frac{\sin x}{(x^2 + 4)} \right|$ $R(x_1) = \left[\frac{(x^2 + 4)\cos x - 2x\sin x}{(x^2 + 4)^2}\right]$ $R(x_1) = \frac{4-0}{16} = \frac{1}{4}$ Residue at $x_2 = 2i$ is given by $R(x_2) = \left| \frac{(x-2i)\sin x}{x^2(x+2i)(x-2i)} \right|_{x=2i}$ $R(x_2) = \frac{\sin 2i}{(2i)^2 \times 4i} = \frac{-\sin 2i}{16i}$ By residue theorem $\oint_{C} f(x) \, dx = 2\pi i \times \big[\Sigma R(x_i) \big]$ $\oint \frac{\sin x}{x^2(x^2+4)} = 2\pi i [R(x_1) + R(x_2)]$ $\oint \frac{\sin x}{x^2(x^2+4)} = 2\pi i \left[\frac{1}{4} - \frac{\sin 2i}{16i} \right]$ $\oint \frac{\sin x}{x^2(x^2+4)} = \frac{\pi i}{2} - \frac{\pi \sin 2i}{8}$ Hence, none of the option is matching. This question is not in proper form as per their options, so this question must be considered as marks to all (MTA). **Question 37 Digital Electronics (1M)** If $(1235)_x = (3033)_y$, where x and y indicate bases of the corresponding numbers, then (A) x = 7 and y = 5(B) x = 8 and y = 6 (C) x = 6 and y = 4(D) x = 9 and y = 7Ans. B Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 www.gateacademy.co.in © Copyright www. Macebook.com/gateacademy Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052





Method 2 :

Given $R_X(\tau)$ can be represented as,

$$R_X(\tau) = 2tri\left(\frac{\tau}{2}\right)$$

Power spectral density of X(t) is related to $R_X(\tau)$ as,

 $S_v(f) = 4\operatorname{sinc}^2(2f)$

$$S_X(f) = \text{F.T.} \left[R_X(\tau) \right]$$
$$2tri\left(\frac{\tau}{2}\right) \xleftarrow{\text{F.T.}} 4\operatorname{sinc}^2(2f)$$

...

 \therefore Average power of X(t)

$$P_x = \int_{-\infty}^{\infty} S_x(f) df = 4 \int_{-\infty}^{\infty} \operatorname{sinc}^2(2f) df$$

$$P_x = 4 \cdot [\text{Energy of } \sin(2f)]$$

From standard result,

Energy of sinc(f) = 1

Using scaling property,

Energy of sinc
$$(2f) = \frac{1}{2}$$

From equation (iii),

$$P_x = 4 \times \frac{1}{2} = 2 \mathrm{W}$$

Hence, average power of X(t) is 2 W.

Question 39

Communications System (2M)

...(iii)

A message signal having peak-to-peak value of 2 V, root mean square value of 0.1 V and bandwidth of 5 kHz is sampled and fed to a pulse code modulation (PCM) system that uses a uniform quantizer. The PCM output is transmitted over a channel that can support a maximum transmission rate of 50 kbps. Assuming that the quantization error is uniformly distributed, the maximum signal to quantization noise ratio that can be obtained by the PCM system (rounded off to two decimal places) is _____.

Ans. 30.72

Sol. Given : Peak to peak value of message signal m(t)

$$V_{P-P} = V_H - V_L = 2 V$$

RMS value of message signal, m(t) = 0.1V

Bandwidth of message signal or maximum frequency component of m(t)

 $f_m = 5 \,\mathrm{kHz}$

© Copyright

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

www.gateacademy.co.in



GATE AC

Bit rate of PCM system $R_b = 50$ kbps

 \therefore Power in message signal m(t)

$$P_{\rm s} = ({\rm RMS \ value})^2 = (0.1)^2 = 0.01 {\rm W}$$

As nothing in mentioned about sampling frequency, so taking Nyquist rate of sampling, i.e.

$$f_s = 2f_m = 10 \,\mathrm{kHz}$$

Bit rate of PCM is, $R_b = nf_s = 50$ kbps

(:: n = Number of bits)

$$\therefore \qquad n = \frac{R_b}{f_s} = 5$$

Given that the PCM system uses uniform quantization and quantization error is uniformly distributed, so Quantization noise power is given as,

$$P_{nq} = \frac{s^2}{12}$$

Where, $s = \text{Step size} = \frac{V_{P-P}}{I}$

L = Number of level $= 2^{n}$

So,

$$P_{nq} = \frac{\left(\frac{V_H - V_L}{2^n}\right)^2}{12} = \frac{\left(\frac{2}{32}\right)^2}{12} = \frac{4}{32 \times 32 \times 12} = \frac{1}{3072}$$

So, the signal to quantization noise power ratio,

 $P_{nq} = \frac{\left(\frac{V_p - V_p}{L}\right)^2}{12}$

$$SN_q R = \frac{P_s}{P_{nq}} = \frac{0.01}{\frac{1}{3072}}$$

 $SN_q R = 30.72$ C C 2 0 4

Hence, the value of signal to quantization noise ratio is 30.72.

Question 40

Communications System (2M)

Consider a polar non-return to zero (NRZ) waveform, using + 2 V and - 2 V for representing binary '1' and '0' respectively, is transmitted in the presence of additive zero-mean white Gaussian noise with variance 0.4 V². If the a priori probability of transmission of a binary '1' is 0.4, the optimum threshold voltage for a maximum a posteriori (MAP) receiver (rounded off to two decimal places) is _____ V.

Ans. 0.04

© Copyright

www.gateacademy.co.in

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



Sol. Given a polar non-return to zero waveform, using +2 V and -2 V for representing binary '1' and '0' respectively is transmitted in presence of white Gaussian noise with variance $0.4V^2$.

$$P(1) = 0.4,$$
 $P(0) = 1 - P(1) = 0.6$

Average probability of error in given as,

$$P_e = P(0)P\left(\frac{1}{0}\right) + P(1)P\left(\frac{0}{1}\right)$$
$$P_e = P(0)\int_{V_{th}}^{\infty} f\left(\frac{z}{0}\right)dz + P(1)\int_{-\infty}^{V_{th}} f\left(\frac{z}{1}\right)dz$$

For probability of error to be minimum, $\frac{dP_e}{dz} = 0$.

$$\begin{split} P(0) \bigg[f\bigg(\frac{z}{0}\bigg) \bigg]_{V_{th}}^{\infty} + P(1) \bigg[f\bigg(\frac{z}{1}\bigg) \bigg]_{-\infty}^{V_{th}} &= 0 \\ -P(0) f\bigg(\frac{z}{0}\bigg) \bigg|_{z=V_{th}} + P(1) f\bigg(\frac{z}{1}\bigg) \bigg|_{V_{th}} &= 0 \\ P(0) f\bigg(\frac{z}{0}\bigg) \bigg|_{z=V_{th}} &= P(1) f\bigg(\frac{z}{1}\bigg) \bigg|_{z=V_{th}} \\ P(0) \cdot \frac{1}{\sqrt{2\pi\sigma_{n}^{2}}} e^{\frac{(z-a_{2})^{2}}{2\sigma_{n}^{2}}} \bigg|_{z=V_{th}} &= P(1) \cdot \frac{1}{\sqrt{2\pi\sigma_{n}^{2}}} e^{\frac{(z-a_{1})^{2}}{2\sigma_{n}^{2}}} \bigg|_{z=V_{th}} \end{split}$$

where, given $a_1 = +2 \text{ V}, a_{12} = -2 \text{ V}$

$$\frac{P(0)}{P(1)} = e^{\frac{(z-a_2)^2}{2\sigma_n^2}} + e^{\frac{(z-a_2)^2}{2\sigma_n^2}} \Big|_{z=V_{th}}$$

On solving, the optimum threshold for MAP receiver is obtained as,

$$V_{th} = \frac{a_1 + a_2}{2} + \frac{\sigma_n^2}{a_1 - a_2} \ln\left(\frac{P(0)}{P(1)}\right) = 2004 \dots (i)$$

Equation (i) may be used as standard equation to find optimum threshold for minimum probability of error

$$(P_e)_{\min}$$
 in MAP receiver : Also, if $P(0) = P(1)$ then $V_{th} = \frac{a_1 + a_2}{2}$

Substituting value of $a_1, a_2, P(0)$ and P(1) in equation (i),

$$V_{th} = \frac{2 + (-2)}{2} + \frac{0.4}{2 - (-2)} \ln\left(\frac{0.6}{0.4}\right)$$
$$V_{th} = \frac{1}{10} \ln(1.5) = 0.0405$$

 Copyright
 Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176
 www.gateacademy.co.in

 Branch Office : Raipur (\$: 79743-90037, Bhopal (\$: 89591-87052)
 www.facebook.com/gateacademy



steps to success.

Hence, the minimum probability of error occurs for the optimum threshold of $V_{th} = 0.0405 \text{ V}$.

Question 41

Communications System (2M)

A digital transmission system uses a (7, 4) systematic linear Hamming code for transmitting data over a noisy channel. If three of the message code-word pairs in this code $(m_i; c_i)$, where, c_i is the code-word corresponding to the i^{th} message m_i , are known to be (1100; 0101100), (1110; 0011110), (0110; 1000110), then which of the following is a **valid code-word** in this code?

(A) 1101001 (B) 1011010 (C) 0001011 (D) 0110100

Ans. C

Sol. Given message and corresponding code-words are,

Message							Code	-word				
m _i	<i>m</i> ₁	<i>m</i> ₂	<i>m</i> ₃	<i>m</i> ₄	P ₁	P ₂	P ₃	<i>m</i> ₁	<i>m</i> ₂	<i>m</i> ₃	<i>m</i> ₄	<i>C</i> _{<i>i</i>}
<i>m</i> ₁₂	1	1	0	0	0	1	0	1	1	0	0	C ₁₂
<i>m</i> ₁₄	1	1	1	0	0	0	1	1	1	1	0	<i>C</i> ₁₄
<i>m</i> ₆	0	1	1	0	1	0	0	0	1	1	0	C_6

Here, m_{12} means, $m_1 m_2 m_3 m_4 = 1100$ and its decimal equivalent is 12

Here, m_{14} means, $m_1 m_2 m_3 m_4 = 1110$ and its decimal equivalent is 14

Here, m_6 means, $m_1 m_2 m_3 m_4 = 0110$ and its decimal equivalent is 6

From four parity generator we have to select any three equation,

 $P_{A} = m_{1} \oplus m_{2} \oplus m_{3}$ $P_{B} = m_{1} \oplus m_{2} \oplus m_{4}$ $P_{C} = m_{2} \oplus m_{3} \oplus m_{4}$ $P_{D} = m_{1} \oplus m_{3} \oplus m_{4}$

From comparing with all three given code-words i.e., C_{12} , C_{14} and C_{6}

$$P_1 = P_B, P_2 = P_C, P_3 = P_A$$

So, for message $m_9 = 1001$, $C_9 = 0111001$

Option (A) is wrong.

 $m_{10} = 1010, C_{10} = 1101010$

Option (B) is wrong.

$$m_{11} = 1011, C_{11} = 0001011$$

Option (C) is correct.

$$m_4 = 0100, C_4 = 1110100$$

Option (D) is wrong.

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success.

Hence, the correct option is (C).

Question 42

Communications System (1M)

GATE AC

A 4 kHz sinusoidal message signal having amplitude 4 V is fed to a delta modulator (DM) operating at a sampling rate of 32 kHz. The minimum step size required to avoid slope overload noise in the DM (rounded off to two decimal places) is _____ V.

Ans. 3.14

Sol. Given : Message signal frequency, $f_m = 4 \text{ kHz}$

Message signal amplitude, $A_m = 4 V$

Sampling rate, $f_s = 32 \,\text{kHz}$

Assume message signal, $m(t) = A_m \cos 2\pi f_m t$

Slope of
$$m(t) = \frac{d}{dt}m(t) = (2\pi f_m)A_m \cos 2\pi f_m t$$

Maximum slope of m(t) is,

$$\left. \frac{d}{dt} m(t) \right|_{\max} = 2\pi f_m A_m \qquad [\because Max]$$

To avoid slope overload distortion,

$$sf_{s} \ge \frac{d}{dt}m(t)\Big|_{\max}$$
$$sf_{s} \ge 2\pi f_{m} A_{m}$$
$$s \ge \frac{2\pi f_{m} A_{m}}{f_{s}}$$

 $\therefore \text{ Maximum value of } (\cos 2\pi f_m t) = 1] \dots (i)$

where, s =Step size.

So, minimum value of step size *s* is,

$$s_{\min} = \frac{2\pi f_m A_m}{f_s}$$
$$s_{\min} = \frac{2\pi \times 4 \times 4}{32} = \pi = 3.14 \text{ V}$$

Hence, the minimum step size required to avoid slope overload is 3.14 V.

Question 43

Communications System (1M)

A speech signal, band limited to 4 kHz, is sampled at 1.25 times the nyquist rate. The speech samples, assumed to be statistically independent and uniformly distributed in the range -5 V to +5 V, are subsequently quantized in an 8-bit uniform quantizer and then transmitted over a voice-grade AWGN telephone channel. If the ratio of transmitted signal power to channel noise power is 26 dB, the minimum channel bandwidth required to ensure reliable transmission of the signal with arbitrarily small probability of transmission error (rounded off to two decimal places) is _____ kHz.

Ans. 9.26

© Convright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
Copyright	Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052	www. Macebook.com/gateacademy



...(i)



Sol. Given :

Speech signal/message signal frequency, $f_m = 4 \text{ kHz}$

Sampling frequency, $f_s = 1.25 f_{NR}$

Nyquist rate $f_{NR} = 2f_m = 2 \times 4 = 8$ kHz

Thus, sampling frequency, $f_s = 1.25 f_{NR} = 1.25 \times 8 \text{ kHz} = 10 \text{ kHz}$

Speech samples are uniformly distributed in the range -5V to 5 V and subsequently quantized in 8-bit uniform quantizer and transmitted over AWGN channel, so number of bits used by quantizer,

i.e.,
$$n = 8$$

Bit rate is given as, $R_b = nf_s = 8 \times 10 = 8$ kbps

According to channel capacity theorem,

$$(R_b)_{\max} \leq C$$

 $(R_b)_{\max} = C = B \log_2(1 + SNR)$

 $80 \times 10^3 = B \log_2(1 + SNR)$

Here, $(SNR)_{dB} = 26 \text{ dB}$

 $10\log_{10}(SNR) = 26$

$$SNR = (10)^{2.6} = 398.1$$

From equation (i),

$$80 \times 10^3 = B \log_2(1 + 398.1)$$

⇒
$$B = \frac{80 \times 10^3}{\log_2(399.1)} = 9.259 \text{ kHz} \approx 9.26 \text{ kHz}$$

Hence, minimum bandwidth required for reliable transmission is 9.259 kHz.

Question 44

Communications System (2M)

A sinusoidal message signal having root mean square value of 4 V and frequency of 1 kHz is fed to phase modulator with phase deviation constant 2 rad/volt. If the carrier signal is $c(t) = 2\cos(2\pi 10^6 t)$, the maximum instantaneous frequency of the phase modulated signal (rounded off to one decimal place) is

Ans.	1011313.71
Sol.	Given :
	Message signal frequency, $f_m = 1 \text{ kHz}$
	Carrier signal, $c(t) = 2\cos(2\pi 10^6 t)$
	Phase sensitivity factor, $k_p = 2 \text{ rad/V}$
	Assuming message signal, $m(t) = A_m \sin(2\pi f_m t)$
	RMS value of message signal $m(t)$ is,
0.0	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176

www. facebook.com/gateacademy







Consider a carrier signal which is amplitude modulated by a single-tone sinusoidal message signal with a modulation index of 50%. If the carrier and one of the sidebands are suppressed in the modulated signal, the percentage of power saved (rounded off to one decimal place) is _____.

Ans. 94.44

Sol. Given signal is single tone sinusoidal message signal with modulation index,

 $\% m_a = 50\%$

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in	
	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. 🛐 acebook.com/gateacademy	

So



GATE ACA steps to success...

 $m_a = 0.5$

According to question, carrier and one side band is suppressed, so saved power is, Power saved = Carrier Power + One side band Power

<u>A</u>R

 $f_{image} = 2 \times 1000 - 600 = 1400 \text{ kHz}$

Hence, the image frequency is 1400 kHz.

Question 47

In a high school having equal number of boy students and girl students. 75% of students study science and remaining 25% students study commerce. Commerce students are two times more likely to be a boy than are science students. The amount of information gained in knowing the a randomly selected girl student studies commerce (rounded off to 3 decimal places) is _____ bits.

Ans. 3.322

Sol. Method 1 :

Given :

50% of the total students are boys so probability of boys $P(B) = \frac{1}{2}$

50% of the total students are girls so probability of girls $P(G) = \frac{1}{2}$

75% students studies science, so probability of student studies science, $P(S) = \frac{3}{4}$

25% students studies commerce, so probability of student studies commerce, $P(C) = \frac{1}{4}$

Given commerce students are two times more likely to be a boy than are science students.

Let the probability that a science student is boy i.e., $P\left(\frac{B}{S}\right) = p$.

Then as given, the probability that a commerce student is boy i.e., $P\left(\frac{B}{C}\right) = 2p$.

From total probability theorem, the probability of a selected student to be a boy is

$$\frac{1}{2} = \left(\frac{1}{4} \times 2p\right) + \left(\frac{3}{4} \times p\right)$$

$$\frac{1}{2} = \frac{5p}{4}$$

$$p = \frac{2}{5}$$
So, $P\left(\frac{B}{S}\right) = p = \frac{2}{5}$ and $P\left(\frac{B}{C}\right) = 2p = \frac{4}{5}$

Hence probability of a selected commerce student is a girl,

$$P\left(\frac{G}{C}\right) = 1 - P\left(\frac{B}{C}\right) = 1 - \frac{4}{5} = \frac{1}{5}$$

 $P(B) = P(C)P\left(\frac{B}{B}\right) + P(S)P\left(\frac{B}{B}\right)$

Probability of randomly selected girl studies commerce is given as

© Copyright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.ir	
	Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052	www. M acebook.com/gateacademy	

Engineering Mathematics (2M)

GATE 2021 [Afternoon Session] **Electronics & Communication Engineering**



GATE A



Hence, information in knowing that a randomly selected girl studies commerce is given as

$$I = \log_2 \left[\frac{1}{P\left(\frac{C}{G}\right)} \right] \text{ bits} = \log_2 10 = 3.32 \text{ bits}$$

Hence, the amount of information gained in knowing the a randomly selected girl student studies commerce is 3.32 bits.

Method 2 :

Let total number of students is 100.

Given, there are equal number of boys and girl students.

Total number of boys = 50*.*..

Total number of girls = 50

Given commerce students are two times more likely to be a boy than are science students.

Let Probability of science student to be boy = p.

Probability of science students to be girl = 1 - p...

p is defined as,

<i>p</i> =	Number of boys in science	B_{s}
	Total students in science	75

- Number of boys in science $= B_s = 75 p$...
- Number of girls in science = 75 75p...

Number of boys in commerce = 50 - 75p

p

Number of girls in commerce = 25 - (50 - 75p) = 75p - 25

Given,
$$\frac{50-75p}{25} = 2$$

 $50-75p = 50p$
 $125p = 50$
 $p = \frac{50}{125} = \frac{2}{5}$

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



- :. Number of girls in commerce = $75p 25 = 75 \times \frac{2}{5} 25 = 30 25 = 5$
- ... Probability that if a randomly selected student out of 100 students is a girl then she studies commerce is,

$$P\left(\frac{C}{G}\right) = \frac{\text{Number of girls in commerce}}{\text{Total girl students}}$$
$$= \frac{5}{50} = \frac{1}{10}$$

Hence, Information in knowing that a randomly selected student is girl and studies commerce is

$$I = \log_2 \frac{1}{P\left(\frac{G}{C}\right)} \text{ bits}$$

 $I = \log_2 10 = 3.32$ bits

Hence, the amount of information gained in knowing the a randomly selected girl student studies commerce is 3.32 bits.

Question 48

Analog Electronics (2M)

An asymmetrical periodic pulse train V_{in} of 10 V amplitude with on-time $T_{ON} = 1$ ms and off-time $T_{OFF} = 1 \ \mu s$ is applied to the circuit shown in figure. The diode D_1 is ideal.



The difference between the maximum voltage and minimum voltage of the output wave form V_0 (in integer) is _____ V.

Ans. 10

Sol. Given circuit and asymmetrical periodic input V_{in} is shown below,



www.gateacademy.co.in



Here, $T_{ON} = 1 \text{ msec}$, $T_{OFF} = 1 \text{ } \mu \text{sec}$ and initially capacitor C is uncharged and diode D is ideal diode.

(i) For $0 < t < T_{ON}$:

Maximum value of V_{in} is 10 V and diode D is ON and will be short circuit, so capacitor will get charged instantly to 10 V as shown below,

GATE AC

stebs to succe



Thus, capacitor voltage $V_c = 10$ V and voltage $V_0 = 0$ volt.

(ii) For $T_{ON} < t < T_{OFF}$:

Given input voltage $V_{in} = 0$ it means short circuit and diode is OFF and will be open circuit, so circuit becomes as,

$$Current, I = \frac{-10}{500} = -20 \text{ mA}$$

$$Voltage, V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$
Thus output waveform under steady state is,
$$V_0 = I \times 500 = (-20) \times 500 = -10 \text{ V}$$

© Copyright

www.gateacademy.co.in Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052

www. facebook.com/gateacademy



Hence, the difference between the maximum voltage and minimum voltage of the output wave form V_0 is + 10 V.

Question 49

Engineering Mathematics (1M)

If the vectors (1.0, -1.0, 2.0) (7.0, 3.0, x) (2.0, 3.0, 1.0) in \mathbb{R}^3 are linearly dependent, the value of x is

Ans. 8

Sol. Given :

According to Question given vectors are (1.0, -1.0, 2.0), (7.0, 3.0, x) and (2.0, 3.0, 1.0) are linearly dependent.

We know that the determinant of linearly dependent vectors are zero.

(6) = 0

$$\begin{vmatrix} 1 & -1 & 2 \\ 7 & 3 & x \\ 2 & 3 & 1 \end{vmatrix} = 0$$

1(3-3x)+1(7-2x)+2(21-
3-3x+7-2x+30=0
5x = 40
x=8

Hence, the correct answer is 8.

Question 50

Electronic Devices (2M)

For an n channel silicon MOSFET with 10 nm gate oxide thickness, the substrate sensitivity $(\partial V_T / \partial |V_{BS}|)$ is found to be 50 mV/V at a substrate voltage $|V_{BS}| = 2V$, where V_T is the threshold voltage of the MOSFET. Assume that $|V_{BS}| >> 2\phi_B$, where $q\phi_B$ is the separation between the fermi

energy level E_F and the intrinsic level E_i in the bulk. Parameters given are :

Electron charge $(q) = 1.6 \times 10^{-19} C$

Vacuum permittivity (ε_0) = 8.85×10⁻¹² F/m

Relative permittivity of silicon $(\varepsilon_{si}) = 12$

Relative permittivity of oxide $(\varepsilon_{ox}) = 4$

The doping concentration of the substrate is

(A)
$$7.37 \times 10^{15} \text{ cm}^{-3}$$

(C) $2.37 \times 10^{15} \text{ cm}^{-3}$

(B) $4.37 \times 10^{15} \text{ cm}^{-3}$ (D) $9.37 \times 10^{15} \text{ cm}^{-3}$

Ans.

Sol. Given :

Gate-oxide thickness, $t_{ox} = 10 \text{ nm}$

© Copyright

www.gateacademy.co.in www.facebook.com/gateacademy

GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success..

Substrate sensitivity, $\frac{\partial V_T}{\partial |V_{rc}|} = 50 \text{ mV/V}$ Substrate voltage, $|V_{BS}| = 2$ V Electron charge $(q) = 1.6 \times 10^{-19} C$ Vacuum permittivity (ε_0) = 8.85×10⁻¹² F/m Relative permittivity of silicon $(\varepsilon_{si}) = 12$ Relative permittivity of oxide $(\varepsilon_{ox}) = 4$ Threshold voltage when body effect is consider, $V_T = V_{To} + \gamma \left| \sqrt{\left| 2\phi_F \right| + \left| V_{SB} \right|} - \sqrt{\left| 2\phi_F \right|} \right|$...(i) Where, $\gamma = \frac{\sqrt{2qN_A\varepsilon_{si}}}{C} = \frac{\sqrt{2qN_A\varepsilon_{si}}}{\varepsilon_{corr}} t_{ox}$ $\begin{bmatrix} \because & C_{ox} = \frac{\varepsilon_{ox}}{t_{ox}} \end{bmatrix}$ As per the question, $\phi_F = \phi_B \rightarrow Both$ are same Differentiate equation (i), with respect to V_{BS} , $\frac{\partial V_T}{\partial V} = 0 + \gamma \frac{1}{2} \left(\left| 2\phi_F \right| + \left| V_{SB} \right| \right)^{-\frac{1}{2}}$...(ii) Since $|V_{SB}| \gg |2\phi_F|$, so equation (ii) becomes as, $\frac{\partial V_{T}}{\partial V_{rs}} = \gamma \left(\frac{1}{2}\right) \left(\left|V_{SB}\right|\right)^{-\frac{1}{2}}$ $50 \times 10^{-3} = \gamma \left(\frac{1}{2}\right) (2)^{-\frac{1}{2}}$ $50 \times 10^{-3} = \gamma \frac{1}{2\sqrt{2}}$ $\gamma = 2\sqrt{2} \times 50 \times 10^{-3} = 0.14142$ e 2 As $\gamma = \sqrt{2qN_A \varepsilon_{si}} \left[\frac{t_{ox}}{\varepsilon} \right]$ $\sqrt{2qN_A\varepsilon_{si}} \times \frac{t_{ox}}{\varepsilon} = 0.14142$ $2q N_A \varepsilon_{si} = \left[0.14142 \times \left(\frac{\varepsilon_{ox}}{t} \right) \right]^2$ $N_A = \frac{1}{2a\epsilon_a} \left[0.14142 \times \left(\frac{\epsilon_{ox}}{t}\right) \right]^2$

© Copyright

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176

www.gateacademy.co.in

GATE 2021 [Afternoon Session] **Electronics & Communication Engineering**



$$N_{A} = \frac{1}{2q(12\epsilon_{0})} \times \left[0.14142 \times \left(\frac{4\epsilon_{0}}{t_{ox}}\right) \right]^{2} \qquad (\because \ \epsilon_{si} = 12\epsilon_{0}, \ \epsilon_{ox})$$
$$N_{A} = \frac{\left(0.14142\right)^{2} \times \left(4 \times 8.85 \times 10^{-14}\right)^{2}}{2 \times 1.6 \times 10^{-19} \times 12 \times 8.55 \times 10^{-14} \times \left(10 \times 10^{-9} \times 100\right)^{2}}$$
$$N_{A} = 7.37 \times 10^{15} \ \text{cm}^{-3}$$

Hence, the correct option is (A).

Question 51

In the circuit shown in the figure, the transistors M_1 and M_2 are operating in saturation. The channel length modulation coefficients of both the transistors are non-zero. The transconductance of the MOSFETs M_1 and M_2 are g_{m1} and g_{m2} , respectively, and the internal resistance of the MOSFETs M_1 and M_2 are r_{01} and r_{02} , respectively.





Analog Electronics (1M)

steps to

 $=4\varepsilon_0$)

www. Macebook.com/gateacademy



steps to success.



i.e.
$$r_{in} \neq 0, r_{in} \neq 0$$

From figure $V_{s_i} = 0$ V, $V_{s_i} = 0$ V and $V_{t_i} = 0$ V,
 $V_{i_1} = V_{t_2} = V_{ui}, V_{s_i} = V_{ui}$.
So, $V_{g_i} = V_{g_i} - V_{i_2} = 0 - V_{out} = -V_{out}$
 $V_{g_{i_1}} = V_{g_i} - V_{i_2} = V - 0 = V_i$
The AC equivalent model of given circuit is shown below,

$$S_1 = V_{g_i} = V_{g$$

www.gateacademy.co.in www. Macebook.com/gateacademy





Method 2 :

Given MOSFET arrangement is shown below,



Channel length modulation coefficient $\lambda \neq 0$, it means internal resistance of MOSFET M_1 and M_2 are not zero i.e., $r_{01} \neq 0$, $r_{02} \neq 0$.

AC equivalent circuit :

- (i) All capacitors are short circuited.
- (ii) All DC voltage sources replaced by ground.





When drain and gate of MOSFET M_1 are shorted to each other then it can be replaced by resistance of

value $\left(\frac{1}{gm_1} || r_{01}\right)$ as shown below,


The circuit in the figure contains a current source driving a load having an inductor and a resistor in series, with a shunt capacitor across the load. The ammeter is assumed to have zero resistance. The switch is closed at time t = 0.



www.gateacademy.co.in

PAGE 75 **GATE 2021** [Afternoon Session] Electronics & Communication Engineering



 $I_{0}(s) = \frac{I_{i}(s) \times \frac{1}{LC}}{s^{2} + \frac{R}{L}s + \frac{1}{LC}}$ $\frac{I_{0}(s)}{I_{i}(s)} = \frac{\frac{1}{LC}}{s^{2} + \frac{R}{L}s + \frac{1}{LC}} \qquad \dots (i)$

Equation (i) shows current transfer function, so we can compare denominator of equation (i) with characteristic equation of second order system $s^2 + 2\xi\omega_n s + \omega_n^2 = 0$, then we get

(i) $\omega_n^2 = \frac{1}{LC}$ $\omega_n^2 = \frac{1}{10 \times 10^{-3} \times 100 \times 10^{-12}}$ $\omega_n = \sqrt{10^{12}} = 10^6 \text{ rad/sec}$ (ii) $2\xi\omega_n = \frac{R}{L}$ $2\xi \times 10^6 = \frac{5000}{10 \times 10^{-3}}$ $\xi = \frac{1}{4} = 0.25$

Here $\xi < 1$ so system is underdamped system.

(iii)Steady state value of $i_0(t)$ is,

$$\lim_{t \to \infty} i_0(t) = i_0(\infty) = \lim_{s \to 0} sI_0(s)$$

$$\lim_{t \to \infty} i_0(t) = i_0(\infty) = \lim_{s \to 0} s \left(\frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}\right)I_i(s)$$

$$\lim_{t \to \infty} i_0(t) = i_0(\infty) = \lim_{s \to 0} s \left(\frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}\right)\left(\frac{1}{s}\right)$$

$$\lim_{t \to \infty} i_0(t) = i_0(\infty) = 1$$

Input $I_i(s) = \frac{1}{s}$ is the step function and $\xi < 1$, so response $i_0(t)$ will be an underdamped response for unit step signal as shown below,

 Copyright
 Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176
 www.gateacademy.co.in

 Branch Office : Raipur (\$) : 79743-90037, Bhopal (\$) : 89591-87052
 www.flacebook.com/gateacademy



PAGE 77 GATE 2021 [Afternoon Session] Electronics & Communication Engineering







Nodal analysis at node V_0

$$-6 + \frac{V_0 - 4}{1} + \frac{V_0}{1} + 8 = 0$$

2V_0 - 10 + 8 = 0
2V_0 = 2
V_0 = 1 V

Hence, the value of V_0 is 1 V.

Question 54

Electromagnetic Theory (2M)

A standard air filled rectangular waveguide with dimensions a = 8 cm, b = 4 cm operates at 3.4 GHz. For the dominant mode of wave propagation, the phase velocity of the signal is v_p . The value (rounded off to two decimal places) of v_p / c , where c denotes the velocity of light is _____.

Ans. 1.198

Sol. Given : a = 8 cm, b = 4 cm,

For a standard rectangular waveguide a > bSo, cut-off frequency for dominant mode (TE_{10}) is

$$f_{c} = \frac{c}{2a}$$

$$f_{c} = \frac{3 \times 10^{8}}{2 \times 8 \times 10^{-2}} = \frac{30 \times 10^{7}}{16 \times 10^{-2}} = 1.875 \times 10^{9} \text{ Hz}$$

$$f_{c} = 1.875 \text{ GHz}$$

Given operating frequency is, f = 3.4 GHz So, phase velocity in rectangular waveguide,

$$v_{p} = \frac{c}{\sqrt{1 - \left(\frac{f_{C}}{f}\right)^{2}}}$$
$$\frac{v_{p}}{c} = \frac{1}{\sqrt{1 - \left(\frac{1.875}{3.4}\right)^{2}}} = 1.198$$

Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052

www.gateacademy.co.in



GATE 2021 [Afternoon Session] Electronics & Communication Engineering



steps to success..

Hence, the value of v_p / c is 1.198.

Question 55

© Copyright

Network Theory (2M)

www. Macebook.com/gateacademy

Consider the two port network shown in the figure.



Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🔇 : 89591-87052

GATE 2021 [Afternoon Session] GATE AC PAGE **Electronics & Communication Engineering** 79 steps to succ Thus admittance parameter of given network is, $[Y] = \begin{bmatrix} 2 & -4 \\ -1 & 2 \end{bmatrix}$ Hence, the correct option is (C). General Aptitude **Question 56 General Aptitude (1M)** p and q are positive integers and $\frac{p}{q} + \frac{q}{p} = 3$, then, $\frac{p^2}{q^2} + \frac{q^2}{p^2} =$ (C) 9 (A) 3 **(B)** 7 (D) 11 Ans. B Given : $\frac{p}{q} + \frac{q}{p} = 3$ Sol. Squaring on both sides, we get $\frac{p^2}{q^2} + \frac{q^2}{p^2} + 2\frac{p}{q}\frac{q}{p} = 9$ $\frac{p^2}{q^2} + \frac{q^2}{p^2} + 2 = 9$ $\frac{p^2}{q^2} + \frac{q^2}{p^2} = 9 - 2 = 7$ Hence, the correct option is (B). **Question 57 General Aptitude (1M)** The current population of a city is 11,02,500. If it has been increasing at the rate of 5% per annum, what was its population 2 years ago? (A) 9, 92, 500 (C) 10, 00, 000 (B) 9, 95, 006 (D) 12, 51, 506 С Ans.

Sol. Given :

Current population of city = 1102500

Rate of increment of population = 5% per year

Method 1 :

Let the population of the city 2 years ago be x. As the population has been increasing at the rate of 5% per annum, so after 2 years x becomes as,

 $(x \times 105\%) \times 105\% = 1102500$

$$x \times \frac{105}{100} \times \frac{105}{100} = 1102500$$
$$x = \frac{1102500 \times 100 \times 100}{105 \times 105}$$

Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176 Branch Office : Raipur 🔇 : 79743-90037, Bhopal 🚫 : 89591-87052

www.gateacademy.co.in



© Copyright

www. facebook.com/gateacademy

PAGE 81 **GATE 2021** [Afternoon Session] Electronics & Communication Engineering





- : Sides of Hexagon formed by an equilateral triangle to the same equilateral triangle =1:3
- ... The ratio of the area of the regular convex Hexagon (*PQRSTU*) to the area of original equilateral triangle is

$$\Rightarrow \quad \frac{3\sqrt{3}}{2}(1)^2 : \frac{\sqrt{3}}{4}(3)^2$$
$$\Rightarrow \quad \frac{3\sqrt{3}}{2} : \frac{9\sqrt{3}}{4}$$
$$\Rightarrow \quad 2:3$$

Hence, the correct option is (A).

Question 59

General Aptitude (2M)

steps to succe

Consider a square sheet of side 1 unit. In the first step, it is cut along the main diagonal to get two triangles. In the next step, one of the cut triangles is revolved about its short edge to from solid cone. The volume of a resulting cone, in a cube units is ______.





GATE 2021 [Afternoon Session] Electronics & Communication Engineering







The number of minutes spent by two Students, *X* and *Y*, exercising every day in a given week are shown in the bar chart above.

The number of days in a given week in which one of the students spent a minimum of 10% more than the other student, on a given day, is

(4	A) 4	(B) 5	(C) 6	(D) 7
_				

Ans. C

PAGE

83

Sol. According to the given data in question we can formed the table as shown below,

Days	Y	X	%more than the other students
Sunday	65	55	65-55
			$\frac{1}{55}$ ×100% = 18.18%
Saturday	50	60	$\frac{60-50}{50} \times 100\% = 20\%$
Friday	35	20	$\frac{35-20}{20} \times 100\% = 75\%$
Thursday	55	60	$\frac{60-55}{55} \times 100\% = 9.09\%$
Wednesday	50	60	$\frac{60-50}{50} \times 100\% = 20\%$
Tuesday	65	55	$\frac{65-55}{55} \times 100\% = 18.18\%$
Monday	70	45	$\frac{70-45}{45} \times 100\% = 55.55\%$



Question 63

General Aptitude (2M)

Computers are ubiquitous. They are used to improve efficiency in almost all fields from agriculture to space exploration. Artificial intelligence (AI) is currently a hot topic. AI enables computer to learn, given enough training data. For humans, sitting in front of a computer for long hours can lead health issues. Which of the following can be deduced from the above passage?

(i) Nowadays computers are present in almost all places.

© Convright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in
Copyright	Branch Office : Raipur 🚫 : 79743-90037, Bhopal 🚫 : 89591-87052	www. Sacebook.com/gateacademy

PAGE 85	G. Ele	ATE 2021 [Afternoon Session] ectronics & Communication Engineering	EACADEMY steps to success				
	 (ii) 0 (iii) 1 (iv) 4 (A) (Computers cannot be used for solving problems in engineering. For humans, there are positive and negative effects of using computers. Artificial intelligence can be done without data. ii) and (iii) (B) (ii) and (iv) (C) (i), (ii) and (iv)	(D) (i) and (iii)				
Ans. Quest	D ion 6/		Conoral Antitudo (2M)				
QUESI	Giver	below are two statements and two conclusions.	deneral Aptitude (2m)				
	Statement :						
	State	nent 1 : All purple are green.					
	State	nent 2 : All Black are green.					
	Conc	lusion :					
	Conc	lusion I : Some black are purple					
	Conc	lusion II : No black is purple					
	Based COR	l on the above statements and conclusions, which one of the follow RECT ?	ving options is logically				
	(A) (Only conclusion I is correct. (B) Only conclusion II is a	correct.				
	(C) I	Either conclusion I or II is correct (D) Both conclusion I & I	I are correct				
Ans.	C						
Sol.	According to the statement and conclusion given in the question we can formed Venn diagram as shown						
	below	Ι,					
	(P) G 1. can't say (wrong)						
		2. can't say (wrong)					
	Both	the conclusion are wrong by can't say condition and variable of the conc	lusion are same Also one				
	concl	usion is positive and another is negative. Hence they full fill the condition	of "either or" case.				
	Henc	e, the correct option is (C).					
Quest	ion 65		General Aptitude (1M)				
	Const	der the following sentences :					
	(i) I woke up from sleep.						
	(ii) I	woked up from sleep.					
	(iii) I	was woken up from sleep.					
	(iv) I was wokened up from sleep.						
	Whice (A)	h of the above sentences are grammatically CORRECT ?	(\mathbf{D}) (i) and (iv)				
Ans	(A) (I R) and (ii) (B) (i) and (iii) (C) (ii) and (iii)	(D) (I) and (IV)				
			~~~				
	vright	Head Office : A/114-115, Smriti Nagar, Bhilai (C.G.), Contact : 9713113156, 9589894176	www.gateacademy.co.in				
Copyright		Branch Office : Raipur 🔇 : 79743-90037. Bhopal 🔇 : 89591-87052	www. Macebook.com/gateacademy				