

General Aptitude Part

Q.1 to Q.5 Carry One Mark Each

Question 1

The village was nested in a green spot, _____ the ocean and the hills.

- (A) through (B) in
(C) at (D) between

Ans. (D)

Sol. The village was nested in a green spot, between the ocean and the hills.
Hence, the correct option is (D).

Question 2

Disagree : Protest :: Agree : _____.

(By word meaning)

- (A) Refuse (B) Pretext
(C) Recommend (D) Refute

Ans. (C)

Sol. Given : disagree is related with protest in a special manner, as disagree is feeling of our choice and protest is resultant action as when we disagree with something we protest against it. In the same relationship agree will be related to recommend.

Here, agree is our internal feeling and recommend is external resultant action as when we are agreed with something we do recommend.

Hence, the correct option is (C).

Question 3

A 'frabjous' number is defined as a 3 digit number with all digits odd, and no two adjacent digits being the same. For example, 137 is a frabjous number, while 133 is not. How many such frabjous numbers exist?

- (A) 125 (B) 720
(C) 60 (D) 80



Ans. (D)**Question 4**

Which one among the following statements must be TRUE about the mean and the median of the scores of all candidates appearing for GATE 2023?

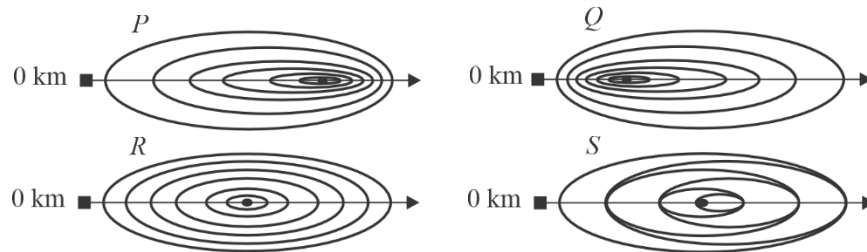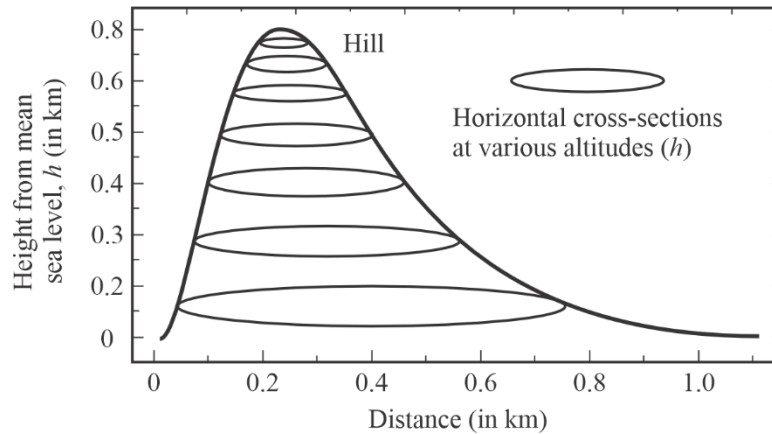- (A) The median is at least as large as the mean.
(B) The mean is at least as large as the median.
(C) At most half the candidates have score that is larger than the median.
(D) At most half the candidates have a score that is larger than the mean.

Ans. (C)**Question 5**

In the given diagram, ovals are marked at different heights (h) of a hill. Which one of the following options P , Q , R and S depicts the top view of the hill?



- (A) P (B) Q
(C) R (D) S

Ans. (B)

Sol. Given : In the diagram ovals (contour lines) are marked at different heights (h) of a hill. The top view of the hill is best depicts by option Q from the figure we can see AB is perpendicular to CD and the slop of the hill is divided in PQ and QR in two parts.

Slop QR is stretching linearly as it down wards and the ovals are widening from line AB towards slop QP , which we can clearly see in the top view diagram of the hill in figure Q .

Hence, the correct option is (B).

Q.6 to Q.10 Carry Two Marks Each

Question 6

Residency is a famous housing complex with many well-established individuals among its residents. A recent survey conducted among the residents of the complex revealed that all of those residents who are well established in their respective fields happen to be academicians. The survey also revealed that most of these academicians are authors of some best-selling books.

Based only on the information provided above, which one of the following statements can be logically inferred with certainty?

- (A) Some residents of the complex who are well established in their fields are also authors of some best-selling books.
(B) All academicians residing in the complex are well established in their fields
(C) Some authors of best-selling books are residents of the complex who are well-established in their fields

$$\begin{bmatrix} 1 & -2 & 1 \\ 1 & 0 & -1 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

On applying the row operation $R_2 \leftarrow R_2 - R_1$, we get

$$\begin{bmatrix} 1 & -2 & 1 \\ 0 & 2 & -2 \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

The modified equations are,

$$x - 2y + z = 0 \quad \dots(i)$$

$$2y - 2z = 0 \quad \dots(ii)$$

At $z = \alpha$,

$$2y - 2\alpha = 0$$

$$y = \alpha$$

$$x - 2\alpha + \alpha = 0 \Rightarrow x = \alpha$$

$$\begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} \alpha \\ \alpha \\ \alpha \end{bmatrix} = \alpha \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}$$

Hence, the correct option is (A).

Question 12

[Measurement]

Inductance of a coil is measured as 10 mH, using an LCR meter, when no other objects are present near the coil. The LCR meter uses a sinusoidal excitation at 10 kHz. If a pure copper sheet is brought near the coil, the same LCR meter will read _____.

- (A) Less than 10 mH
- (B) 10 mH
- (C) More than 10 mH
- (D) Less than 10 mH initially and then stabilizes to more than 10 mH

Ans. (A)

Question 13

[Measurement]

Which of the following flow meters offers the lowest resistance to the flow?

- (A) Turbine flow meter
- (B) Orifice flow meter
- (C) Venturi meter
- (D) Electromagnetic flow meter

Ans. (D)

Question 14

Pair the quantities (p) to (s) with the measuring devices (i) to (iv)

(i)	Linear Variable Differential Transformer (LVDT)	(p)	Torque
-----	---	-----	--------

(ii)	Thermistor	(q)	Pressure
(iii)	Strain gauge	(r)	Linear position
(iv)	Diaphragm	(s)	Temperature

- (A) (i)-(r), (ii)-(s), (iii)-(q), (iv)-(p) (B) (i)-(p), (ii)-(s), (iii)-(r), (iv)-(q)
 (C) (i)-(r), (ii)-(s), (iii)-(p), (iv)-(q) (D) (i)-(q), (ii)-(s), (iii)-(p), (iv)-(r)

Ans. (C)**Question 15**

Capacitance 'C' of a parallel plate structure is calculated as 20 pF using $C = \frac{\epsilon_0 \epsilon_r A}{d}$, where ϵ_0 is the permittivity of free space, ϵ_r is the relative permittivity of the dielectric, A is the overlapping area of the electrodes and d is the distance between them. The value of C is then measured using an LCR meter. If the meter is assumed to be ideal and in produces no error due to cable capacitance, which one of the following needing is likely to be correct?

- (A) 20.5 pF (B) 20 pF
 (C) 19.5 pF (D) 10 pF

Ans. (A)**Question 16****(Digital Electronics)**

The table shows the present state $Q(t)$, next state $Q(t+1)$, and the control input in a flip flop. Identify the flip-flop.

$Q(t)$	$Q(t+1)$	Input
0	0	0
0	1	1
1	0	1
1	1	0

- (A) T flip-flop (B) D flip-flop
 (C) SR flip-flop (D) JK flip-flop

Ans. (A)

Sol. Given : Table of present state $Q(t)$, next state $Q(t+1)$ and control input is shown below,

$Q(t)$	$Q(t+1)$	Input
0	0	0
0	1	1
1	0	1
1	1	0

From the given table, $Q(t+1) = Q(t) \oplus \text{Input} \dots(i)$

Comparing equation (i) with characteristics equation of T-flip-flop.

$$Q(t+1) = Q(t) \oplus T$$

Hence, it is a T flip-flop.

Hence, the correct option is (A).

Question 17**(Digital Electronics)**

Match the Exclusive-OR (XOR) operations (i) to (iv) with the results (p) to (s), where X is a Boolean input.

- (i) $X \oplus X$ (p) 1
 (ii) $X \oplus \bar{X}$ (q) 0
 (iii) $X \oplus 0$ (r) \bar{X}
 (iv) $X \oplus 1$ (s) X

- (A) (i)-(q), (ii)-(r), (iii)-(s), (iv)-(p) (B) (i)-(q), (ii)-(r), (iii)-(p), (iv)-(s)
 (C) (i)-(p), (ii)-(s), (iii)-(q), (iv)-(r) (D) (i)-(q), (ii)-(p), (iii)-(s), (iv)-(r)

Ans. (D)**Sol.** For XOR gate, we know that,

$$A \oplus B = \bar{A}B + A\bar{B}$$

Solving all the given equations using this result of XOR gate,

$$X \oplus X = \bar{X}X + X\bar{X} = 0 + 0 = 0$$

$$X \oplus \bar{X} = \bar{X}\bar{X} + X\bar{X} = X + \bar{X} = 1$$

$$X \oplus 0 = \bar{X}0 + X\bar{0} = X$$

$$X \oplus 1 = \bar{X}1 + X\bar{1} = \bar{X}$$

So, (i)-q, (ii)-p, (iii)-s, (iv)-r.

Hence, the correct option is (D).

Question 18

A light emitting diode (LED) emits light when it is _____biased. A photodiode provides maximum sensitivity to light when it is _____ biased.

- (A) forward, forward (B) forward, reverse
 (C) reverse, reverse (D) reverse, forward

Ans. (B)**Sol.** LED emits light in the forward biased.

Photodiode provides maximum sensitivity to light in reverse biased.

Hence, the correct option is (B).

Question 19

$F(z) = \frac{1}{1-z}$, when expanded as a power series around $z = 2$, would result in $F(z) = \sum_{k=0}^{\infty} a_k (z-2)^k$, with

the region of convergence (ROC) $|z-2| < 1$. The coefficients $a_k, k \geq 0$, are given by the expression_____.

- (A) $(-1)^k$ (B) $(-1)^{k+1}$

(C) $\left(\frac{1}{2}\right)^k$

(D) $\left(\frac{-1}{2}\right)^{k+1}$

Ans. (B)

Sol. Given : $F(z) = \frac{1}{1-z}$

Let $z - 2 = t$

$z = 2 + t$

$$F(t) = \frac{1}{1-2-t} = \frac{1}{-1-t} = \frac{-1}{1+t}$$

$$F(t) = (-1)(1-t+t^2-t^3+\dots)$$

$$F(t) = -1+t-t^2+t^3\dots$$

$$F(z) = -1+(z-2)-(z-2)^2+(z-2)^3+\dots$$

$$F(z) = \sum_{k=0}^{\infty} (-1)^{k+1} (z-2)^k$$

$$\therefore a_k = (-1)^{k+1}$$

Hence, the correct option is (B).

Question 20**[Engineering Mathematics, Differential Equation]**The solution $x(t)$, $t \geq 0$, to the differential equation $\ddot{x} = -k\dot{x}$, $k > 0$ with initial condition $x(0) = 1$ and $\dot{x}(0) = 0$ is

(A) $x(t) = 2e^{-kt} + 2kt - 1$

(B) $x(t) = 2e^{-kt} - 1$

(C) $x(t) = 1$

(D) $x(t) = 2e^{-kt} - kt - 1$

Ans. (C)**Sol. Method 1 :****Given :** Differential equation is, $\ddot{x} = -k\dot{x}$ Initial conditions, $x(0) = 1$, $x'(0) = 0$

$$\frac{d^2x(t)}{dt^2} = -k \frac{dx(t)}{dt}$$

Taking Laplace transform on both sides,

$$s^2X(s) - sx(0) - x'(0) = -k[sX(s) - x'(0)]$$

$$s^2X(s) - s \times 1 - 0 = -k[sX(s) - 1]$$

$$s^2X(s) - s = -ksX(s) + k$$

$$[s^2 + ks]X(s) = s + k$$

$$X(s) = \frac{s+k}{s(s+k)} = \frac{1}{s}$$

Taking inverse Laplace transform,

$$x(t) = 1$$

Hence, the correct option is (C).

Method 2 :

Given : Differential equation is, $\ddot{x} = -k\dot{x}$

$$D^2 = -kD$$

$$D(D+k) = 0$$

$$D = 0, D = -k$$

$$x(t) = C_1 + C_2 e^{-kt} \quad \dots(i)$$

Initial condition, $x(0) = 1$

$$1 = C_1 + C_2 \quad \dots(ii)$$

$$\dot{x}(t) = 0 + C_2(-k)e^{-kt}$$

Also, $\dot{x}(0) = 0 \Rightarrow 0 = C_2 e^0 \Rightarrow C_2 = 0$

From equation (ii), $C_1 = 1$

From equation (i), $x(t) = 1$

Hence, the correct option is (C).

Question 21

(Signals & Systems)

A system has the transfer function $\frac{Y(s)}{X(s)} = \frac{s - \pi}{s + \pi}$. Let $u(t)$ be the unit step function. The input $x(t)$ that results in a steady-state output $y(t) = \sin \pi t$ is _____.

(B) $x(t) = \sin(\pi t) u(t)$

(B) $x(t) = \sin\left(\pi t + \frac{\pi}{2}\right) u(t)$

(C) $x(t) = \sin\left(\pi t - \frac{\pi}{2}\right) u(t)$

(D) $x(t) = \cos\left(\pi t + \frac{\pi}{4}\right) u(t)$

Ans. (C)

Sol. Given : Transfer function of system is, $\frac{Y(s)}{X(s)} = \frac{s - \pi}{s + \pi}$

Steady state output, $y(t) = \sin \pi t$ (Here, $\omega = \pi$ rad/sec)

Transfer function, $H(s) = \frac{s - \pi}{s + \pi}$

Put $s = j\omega$,

$$\Rightarrow H(j\omega) = \frac{j\omega - \pi}{j\omega + \pi}$$

$$\Rightarrow |H(j\omega)| = \frac{\sqrt{\omega^2 + \pi^2}}{\sqrt{\omega^2 + \pi^2}} = 1$$

$$\angle H(j\omega) = 180^\circ - 2 \tan^{-1} \frac{\omega}{\pi}$$

$$\angle H(j\omega)\big|_{\omega=\pi} = 180 - 2 \tan^{-1} 1 = 90^\circ$$

Since, given output, $y(t) = \sin \pi t$

Therefore, input $x(t)$ is,

$$x(t) = \sin(\pi t - 90^\circ)$$

$$\therefore x(t) = \sin\left(\pi t - \frac{\pi}{2}\right)u(t)$$

Hence, the correct option is (C).

Question 22**(Digital Electronics)**

Choose the fastest logic family among the following :

- (A) Transistor-Transistor Logic (B) Emitter-Coupled Logic
(C) CMOS Logic (D) Resistor-Transistor Logic

Ans. (B)

Sol. Emitter coupled Logic is the fastest Logic family among the given options.

Hence, the correct option is (B).

Question 23**[Engineering Mathematics, Limit & Series]**

What is $\lim_{x \rightarrow 0} f(x)$, where $f(x) = x \sin \frac{1}{x}$?

- (A) 0 (B) 1
(C) ∞ (D) Limit does not exist

Ans. (A)

Sol. Given : $f(x) = x \sin \frac{1}{x}$

$$\lim_{x \rightarrow 0} f(x) = \lim_{x \rightarrow 0} x \sin \frac{1}{x}$$

Range of sin function will always be $[-1, 1]$.

$$\therefore \lim_{x \rightarrow 0} x \sin \frac{1}{x} = 0 \times [-1, 1] = 0$$

Hence, the correct option is (A).

Question 24**[Control System, Routh's Array]**

The number of zeros of the polynomial $P(s) = s^3 + 2s^2 + 5s + 80$ in the right half plane is _____.

Ans. 2 (2 to 2)

Sol. Given : Polynomial, $P(s) = s^3 + 2s^2 + 5s + 80$

Routh tabulation of $P(s)$,

s^3	1	5
s^2	2	80
s^1	-35	
s^0	80	

2 sign changes

Since, there are 2 sign changes in the first column of Routh tabulation. The number of zeros in the right half of s-plane will be 2.

Hence, the correct answer is 2.

Question 25

[Control System]

The number of times the Nyquist plot of $G(s)H(s) = \frac{1(s-1)(s-2)}{2(s+1)(s+2)}$ encircles the origin is _____.

Ans. 2 (2 to 2)

Sol. Given : $G(s)H(s) = \frac{(s-1)(s-2)}{(s+1)(s+2)}$

Number of encirclement about origin

$N(0,0)$ = open loop poles in the right half of s-plane open loop zero's in the right half of s-plane.


= $0 - 2 = -2 = 2$ [in clockwise direction]

Hence, the correct answer is 2.

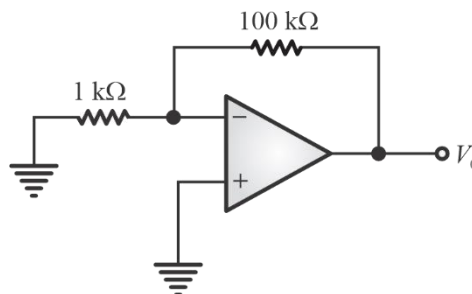Question 26

[Analog Electronics, Op-Amp]

The op-amp in the circuit shown is ideal, except that it has an input bias current of 1 nA and an input offset voltage of $10\mu\text{V}$. The resulting worst-case output voltage will be \pm _____ μV (rounded off to the nearest integer).




Ans. 1110 (1110 to 1110)

Sol. Given : Input bias current = 1 nA

Input offset voltage = $10\mu\text{V}$

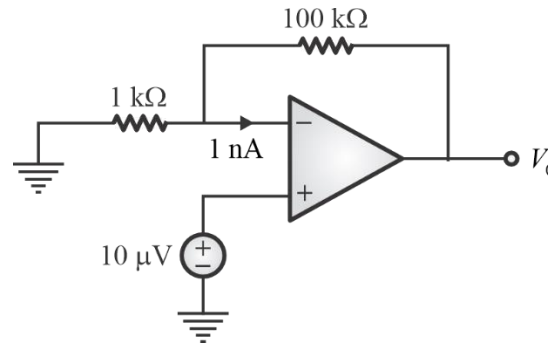Given circuit can be drawn as shown below,



Applying KCL at inverting terminal,

$$\frac{10 \times 10^{-6} - 0}{1 \text{ k}\Omega} + \frac{10 \times 10^{-6} - V_0}{100 \text{ k}\Omega} + 10^{-9} = 0$$

$$\frac{1000 \times 10^{-6} + 10 \times 10^{-6} - V_0}{100 \text{ k}\Omega} = -10^{-9}$$

$$V_0 = 1010 \times 10^{-6} + 10^2 \times 10^{-9} \times 10^3$$

$$V_0 = 1110 \mu\text{V}$$

Hence, the correct answer is 1110.

Question 27

The force per unit length between two infinitely long parallel conductors, with a gap of 2 cm between them is $10 \mu\text{N/m}$. When the gap is doubled, the force per unit length will be ____ $\mu\text{N/m}$ (rounded off to one decimal place).

Ans. 5 (4.9 to 5.1)

Sol. Given : Gap = 2 cm and Force per unit length $F = 10 \mu\text{N/m}$

For two infinitely long,

$$\text{Parallel conductors, } F \propto \frac{1}{\text{gap}}$$

$$\frac{F_1}{F_2} = \frac{(\text{gap})_2}{(\text{gap})_1}$$

$$\Rightarrow \frac{10}{F_2} = \frac{4}{2} \quad (\because \text{Gap is doubled})$$

$$\Rightarrow F_2 = \frac{20}{4} = 5 \mu\text{N/m.}$$

Hence, the correct answer is 5.

Question 28

(Signals & Systems)


Consider the discrete time signal $x[n] = u[-n+5] - u[n+3]$, where $u[n] = \begin{cases} 1; & n \geq 0 \\ 0; & n < 0 \end{cases}$.

The smallest n for which $x[n] = 0$ is _____.

Ans. - 3 (- 3 to - 3)

Sol. Given : $x(n) = u(-n+5) - u(n+3)$

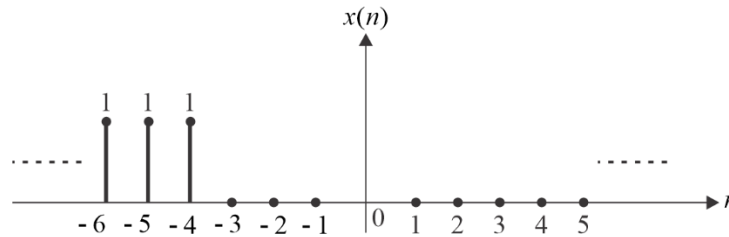The signal $x(n)$ can be plotted as shown below,



So, the smallest value of n is -3 for $x(n)$ to be zero.

Hence, the correct answer is - 3.

Question 29

[Signal & System, Basic of Signal]

Let $y(t) = x(4t)$, where $x(t)$ is a continuous-time periodic signal with fundamental period of 100 s. The fundamental period of $y(t)$ is _____s. (rounded off to the nearest integer)

Ans. 25 (25 to 25)

Sol. Given : $y(t) = x(4t)$

Fundamental period of $x(t) = 100$ s

If $x(t)$ has time period T , then $x(at)$ will have the time period $\frac{T}{a}$.


\therefore Time period of $y(t)$ will be, $T_y = \frac{100}{4} = 25$ sec.

Hence, the correct answer is 25.

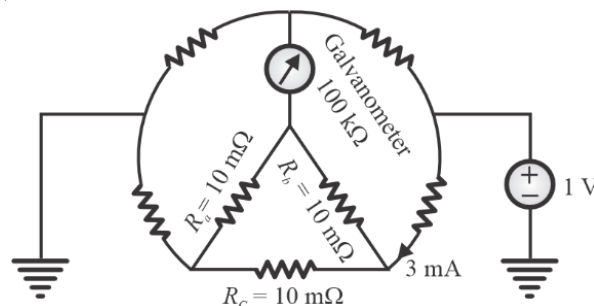Question 30


[Network Theory]

When the bridge given below is balanced, the current through the resistor R_a is _____mA (rounded off to two decimal places).




Ans. 1 (0.99 to 1.01)

Sol. Given circuit is as shown below,

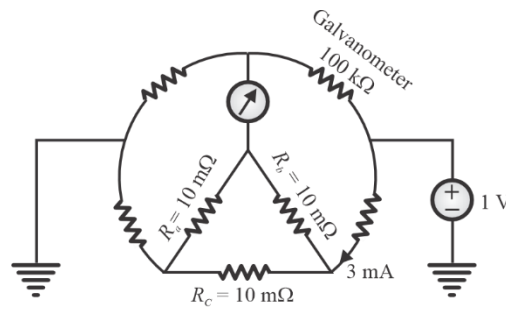

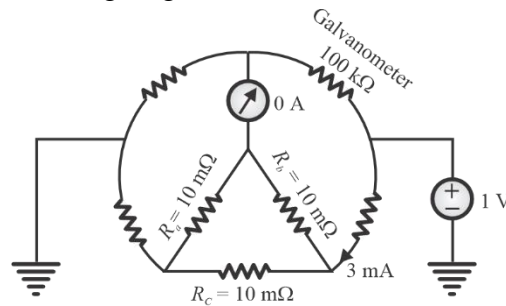As the bridge is balanced, the reading of galvanometer will be zero.




Using current division rule, current through R_a will be, $\frac{3 \times 10}{30} = 1 \text{ mA}$.

Hence, the correct answer is 1.

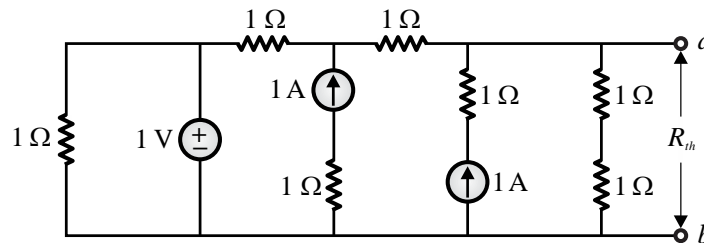
Question 31

In the circuit given, the Thevenin equivalent resistance R_{th} across the terminals 'a' and 'b' is _____ Ω (rounded off to one decimal place).




Ans. 1 (1.0 to 1.0)

Sol. Given circuit is as shown below,

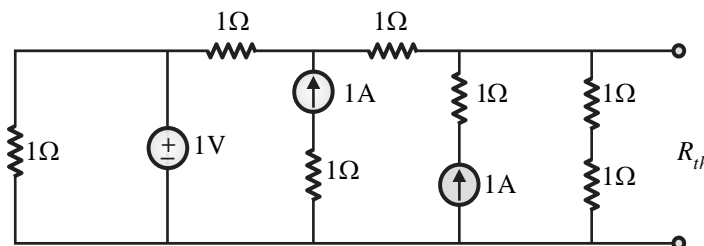

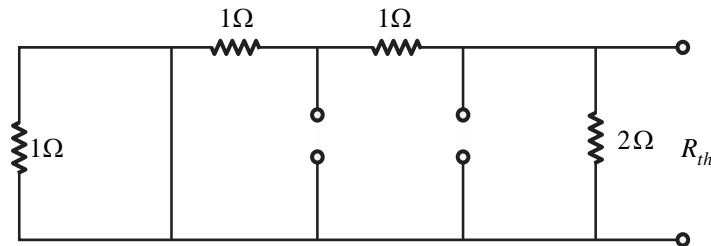For calculating R_{th} , independent sources are replaced by their internal resistance i.e. voltage source is replaced by short circuit and current source by open circuit. Hence, the circuit becomes,



$$R_{th} = 2 \parallel 2$$

$$R_{th} = 1 \Omega$$

Hence, the correct answer is 1.

Question 32

[Engineering Mathematics, Probability & Statics]

X is a discrete random variable which takes values 0, 1 and 2. The probabilities are $P(X = 0) = 0.25$ and $P(X = 1) = 0.5$. With $E[\cdot]$ denoting the expectation operator, the value of $E[X] - [X^2]$ is _____ (rounded off to one decimal places).

Ans. - 0.5 (- 0.5 to - 0.5)

Sol. Given : Data in the question can be tabulated as shown below,

X	0	1	2
$P(X)$	0.25	0.5	0.25

$$\Rightarrow E(X) = \sum X \cdot P(X) = 0(0.25) + 1(0.5) + 2(0.25) = 0.5 + 0.5 = 1$$


$$E(X^2) = \sum X^2 \cdot P(X) = 0^2(0.25) + (1)^2(0.5) + 2^2(0.25) = 1 + 0.5 = 1.5$$

$$E(X) - E(X^2) = 1 - 1.5 = -0.5$$

Hence, the correct answer is - 0.5.

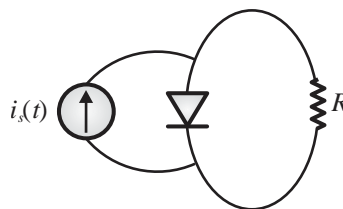Question 33


The diode in the circuit is ideal. The current source $i_s(t) = \pi \sin(3000\pi t)$ mA. The magnitude of average current flowing through the resistor R is _____ mA (rounded off to two decimal places).




Ans. 1 (0.95 to 1.05)

Sol. Given : $i_s(t) = \pi \sin(3000\pi t)$ mA

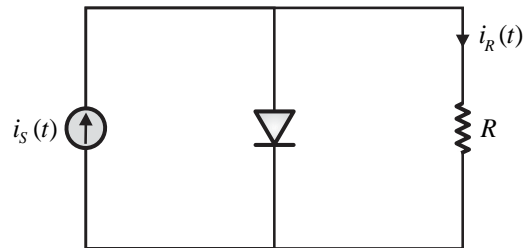Given circuit can be drawn as shown below




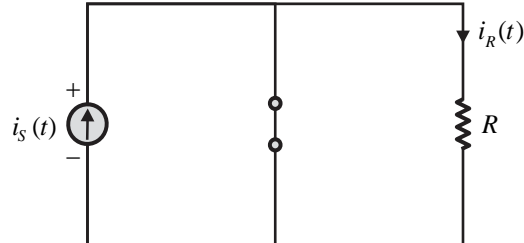For positive half cycle, diode is forward biased (acts as short circuit).




$$\therefore i_R(t) = 0A$$

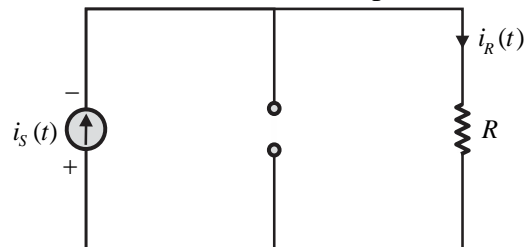For negative half cycle, diode is reverse biased (acts as open circuit),



$$\therefore i_R(t) = -i_s(t)$$

Waveform of $i_R(t)$ will be

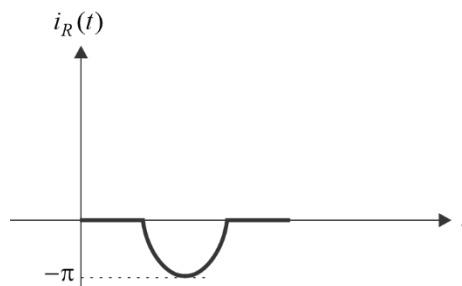

\therefore Average value of $i_R(t)$ will be,

$$(i_R(t))_{avg} = \frac{\text{Peak value}}{\pi} = \frac{-\pi}{\pi} = -1 \text{ mA}$$

Magnitude of average current flowing through R ,

$$|i_R(t)_{avg}| = 1 \text{ mA}$$

Hence, the correct answer is 1.

Question 34

[Measurement]

∴ For input $x(t) = \cos\left(\frac{7\pi}{4}t\right)$, output will be

$$y(t) = H\left(j\frac{7\pi}{4}\right)x(t)$$

$$y(t) = 0.5 \cos\left(\frac{7\pi}{4}t\right)$$

Hence, the correct option is (A).

Question 37**(Signals & Systems)**

The Laplace transform of the continuous-time signal $x(t) = e^{-3t}u(t-5)$ is _____, where $u(t)$ denotes the continuous-time unit step signal.

(A) $\frac{e^{-5s}}{s+3}, \text{Real}\{s\} > -3$

(B) $\frac{e^{-5(s-3)}}{s-3}, \text{Real}\{s\} > 3$

(C) $\frac{e^{-5(s+3)}}{s+3}, \text{Real}\{s\} > -3$

(D) $\frac{e^{-5(s-3)}}{s+3}, \text{Real}\{s\} > -3$

Ans. (C)**Sol. Given :** $x(t) = e^{-3t}u(t-5)$

$$x(t) = e^{-3(t-5+5)}u(t-5)$$

$$x(t) = e^{-15}e^{-3(t-5)}u(t-5)$$

Taking Laplace transform on both sides, we get

$$X(s) = e^{-15} \frac{e^{-5s}}{s+3} = \frac{e^{-5(s+3)}}{s+3}, \quad \text{Real}(s) > -3$$

Hence, the correct option is (C).

Question 38

In a p-i-n photodiode, a pulse of light containing 8×10^{12} incident photons at wavelength $\lambda_0 = 1.55 \mu\text{m}$ gives rise to an average 4×10^{12} electrons collected at the terminals of the device. The quantum efficiency of the photodiode at this wavelength is _____ %.

(A) 50

(B) 54.2

(C) 62.5

(D) 80

Ans. (A)

Sol. Given : Number of electrons collected = 4×10^{12} and number of incident photons = 8×10^{12}
Quantum efficiency,

$$\eta = \frac{\text{Number of electrons collected}}{\text{Number of incident photons}} \times 100$$

$$\eta = \frac{4 \times 10^{12}}{8 \times 10^{12}} \times 100 = 50\%$$

Hence, the correct option is (A).

Question 39

[Engineering Mathematics, Complex Variable]

Let $f(z) = j \left(\frac{1-z}{1+z} \right)$, where z denotes a complex number and j denotes $\sqrt{-1}$. The inverse function

$f^{-1}(z)$ maps the real axis to the _____.

- (A) Unit circle with centre at the origin
(B) Unit circle with centre not at the origin
(C) imaginary axis
(D) real axis

Ans. (A)

Sol. Given : $f(z) = j \frac{1-z}{1+z} = j \left(\frac{1-x-jy}{1+x+jy} \right)$

$$u + jv = \frac{j(1-x) + y}{(1+x) + jy} \cdot \frac{(1+x) - jy}{(1+x) - jy}$$

$$u + jv = \frac{y(1+x) + y(1-x)}{(1+x)^2 + y^2} + j \frac{(1-x^2) - y^2}{(1+x)^2 + y^2}$$

Image of real axis in w plane is

$$v = 0$$

$$\frac{(1-x^2) - y^2}{(1+x)^2 + y^2} = 0$$

$$(1-x^2) - y^2 = 0$$

$$1 = x^2 + y^2$$

∴ Unit circle with center at the origin.

Hence, the correct option is (A).

Question 40

(Digital Electronics)


The simplified form of the Boolean function $F(W, X, Y, Z) = \Sigma(4, 5, 10, 11, 12, 13, 14, 15)$ with the minimum number of terms and smallest number of literals in each term is _____.

- (A) $WX + \bar{W}X\bar{Y} + W\bar{X}Y$
(B) $WX + WY + X\bar{Y}$
(C) $X\bar{Y} + WY$
(D) $\bar{X}Y + \bar{W}Y$

Ans. (C)

Sol. Given : $F(W, X, Y, Z) = \Sigma(4, 5, 10, 11, 12, 13, 14, 15)$

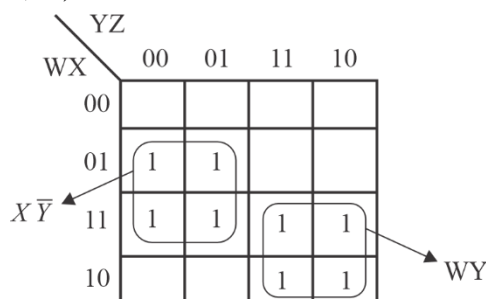K-map of function $F(W, X, Y, Z)$ is shown below,




$$\therefore F(W, X, Y, Z) = X\bar{Y} + WY$$

Hence, the correct option is (C).

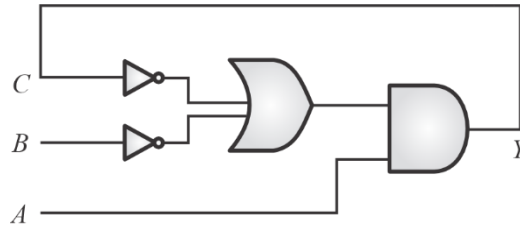Question 41

[Digital Electronics]


For the given digital circuit, $A = B = 1$. Assume that AND, OR and NOT gates have propagation delays of 10ns, 10ns, and 5ns respectively. All lines have zero propagation delay. Given that $C=1$ when the circuit is turned on, the frequency of steady state oscillations of the output Y is _____.



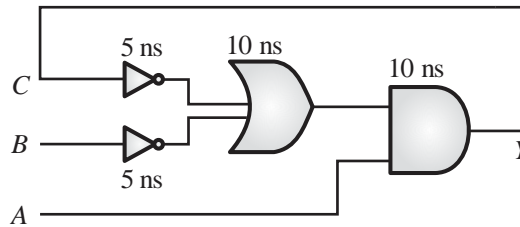- (A) 20 MHz
- (B) 15 MHz
- (C) 40 MHz
- (D) 50 MHz

Ans. (A)


Sol. Given circuit is as shown below with the propagation delay of gates.



Overall propagation delay of the circuit = $5\text{ns} + 10\text{ns} + 10\text{ns} = 25\text{ns}$

\therefore Output Y will toggle for every 25 ns.

The waveform at Y will be,

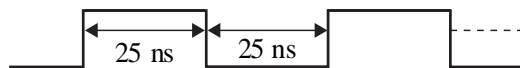

Time period, $T = 50 \text{ ns}$

$$\text{Frequency, } f = \frac{1}{T} = \frac{1}{50 \text{ ns}} = 20 \text{ MHz}$$


Hence, the correct option is (A).

Question 42

[Digital Electronics]

In the circuit shown, the initial binary content of shift register A is 1101 and that of shift register B is 1010. The shift registers are positive edge triggered, and the gates have no delay.

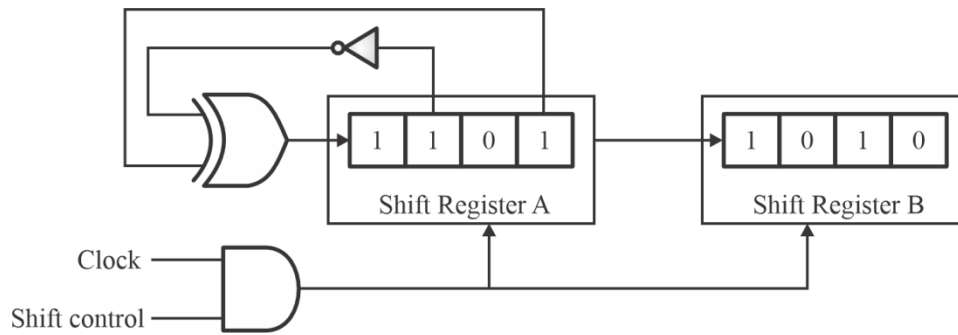When the shift control is high, what will be the binary content of the shift registers A and B after four clock pulses?



(A) $A = 1101, B = 1101$


(B) $A = 1110, B = 1001$

(C) $A = 0101, B = 1101$

(D) $A = 1010, B = 1111$

Ans. (C)

Sol. Given circuit is shown below,

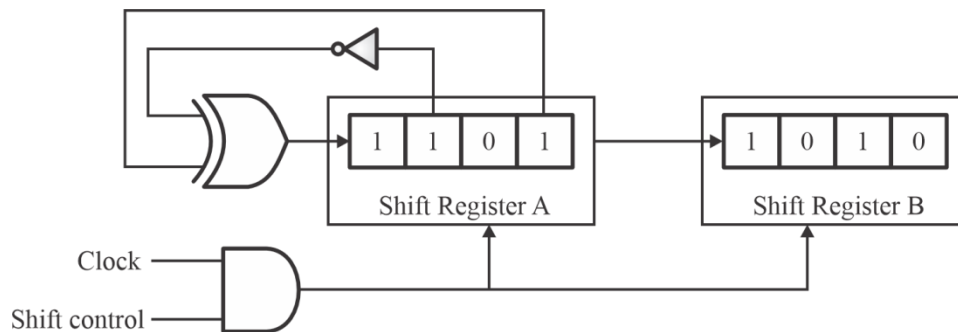

From the given circuit,

Input to shift register, $A = \bar{A}_2 \oplus A_0$

Truth table for the given circuit is shown below,


Clk	$\bar{A}_2 \oplus A_0$	$A_3 A_2 A_1 A_0$	$B_3 B_2 B_1 B_0$
—	1	1 1 0 1	1 0 1 0
1	0	1 1 1 0	1 1 0 1
2	1	0 1 1 1	0 1 1 0
3	0	1 0 1 1	1 0 1 1
4	0	0 1 0 1	1 1 0 1

So, after four clock pulses, $A = 0101$ and $B = 1101$

Hence, the correct option is (C).

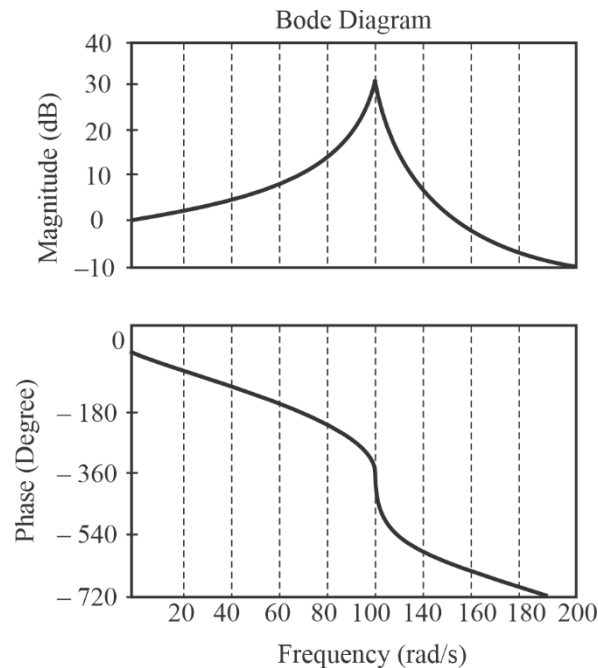Question 43

The magnitude and phase plots shown in the figure match with the transfer function_____.



(B) $\frac{10000}{s^2 + 2s + 10000}$

(B) $\frac{10000}{s^2 + 2s + 10000} e^{-0.05s}$

(C) $\frac{10000}{s^2 + 2s + 10000} e^{-0.5 \times 10^{-12}s}$

(D) $\frac{100}{s^2 + 2s + 100}$

Ans. (B)**Sol.** From the bode plot, the natural frequency $\omega_n = 100$ rad/sec.Phase at $\omega_n = 100$ rad/sec is $\phi = -360^\circ$.

So, option (B) will be the approximate answer.

Hence, the correct option is (B).

Question 44**[Signals & Systems, Fourier Transform]**

A Continuous real valued signal $x(t)$ has finite positive energy and $x(t) = 0, \forall t < 0$. From the list given below, select **ALL** the signals whose continuous-time Fourier transform is purely imaginary.

(A) $x(t) + x(-t)$

(B) $x(t) - x(-t)$

(C) $j(x(t) + x(-t))$

(D) $j(x(t) - x(-t))$

Ans. (B), (C)**Sol. Given :** $x(t)$ is a real signal having finite positive energy and $x(t) = 0, \forall t < 0$.**Consider option (A) :**

Let $y(t) = x(t) + x(-t)$ (i)

$y(-t) = x(-t) + x(t)$ (ii)

From equations (i) and (ii),

$y(-t) = y(t)$

Also, $y(t)$ is a real function

$\therefore y(t)$ is real and even function. So, fourier transform of $y(t)$ will be Real and even function.

So, option (A) is incorrect.

Consider option (B) :

$$\text{Let } y(t) = x(t) - x(-t) \quad \dots(i)$$

$$y(-t) = x(-t) - x(t)$$

$$y(-t) = -[x(t) - x(-t)] \quad \dots(ii)$$

From equation (i) and (ii),

$$y(-t) = -y(t)$$

Also, $y(t)$ is a real function

$\therefore y(t)$ is real and odd function

So, Fourier transform of $y(t)$ will be imaginary and odd function.

So, option (B) is correct.

Consider option (C) :

$$\text{Let } y(t) = j[x(t) + x(-t)] \quad \dots(i)$$

$$y(-t) = j[x(-t) + x(t)] \quad \dots(ii)$$

From equation (i) and (ii),

$$y(-t) = y(t)$$

Also, $y(t)$ is an imaginary function

$\therefore y(t)$ is imaginary and even function

So, Fourier transform of $y(t)$ will be imaginary and even function

So, option (C) is correct.

Consider option (D) :

$$\text{Let } y(t) = j[x(t) - x(-t)] \quad \dots(i)$$

$$y(-t) = j[x(-t) - x(t)]$$

$$y(-t) = -j[x(t) - x(-t)] \quad \dots(ii)$$

From equation (i) and (ii),

$$y(-t) = -y(t)$$

Also, $y(t)$ is an imaginary function,

$\therefore y(t)$ is imaginary and odd function.

So, Fourier transform of $y(t)$ will be real and odd function.

So, option (D) is incorrect.

Hence, the correct options are (B) and (C).

Question 45

A silica-glass fiber has a core refractive index of 1.47 and a cladding refractive index of 1.44. If the cladding is completely stripped out and the core is dipped in water having a refractive index of 1.33, the numerical aperture of the modified fiber is _____ (rounded off to three decimal places).

Ans. 0.626 (0.620 to 0.640)

Sol. Given : Refractive index of core (n_1) = 1.47 and refractive index of cladding (n_2) = 1.44

Now, the cladding is completely stripped out and the core is dipped in water of refractive index 1.33

∴ Modified value of n_2 will be $n_2^1 = 1.33$


$$\text{Modified numerical aperture} = \sqrt{n_1^2 - (n_2^1)^2} = \sqrt{(1.47)^2 - (1.33)^2} = 0.626$$

Hence, the correct answer is 0.626.

Question 46

[Network Theory, Resonance]


In the circuit shown, $\omega = 100\pi$ rad/s, $R_1 = R_2 = 2.2\Omega$ and $L = 7$ mH. The capacitance C for which Y_{in} is purely real is _____ mF (rounded off to two decimal places).

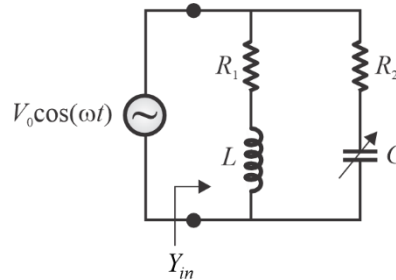

Ans. 1.44 (1.40 to 1.50)

Sol. Given : $\omega = 100\pi$ rad/s, $R_1 = R_2 = 2.2\Omega$ and $L = 7$ mH.

Given circuit is shown below,

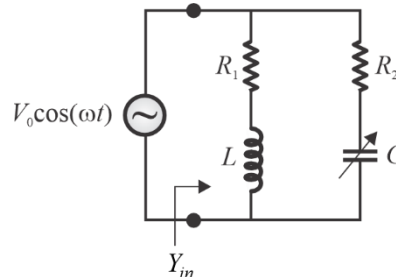

Input admittance of given circuit is,

$$Y_{in} = \frac{1}{R_1 + j\omega L} + \frac{1}{R_2 + \frac{1}{j\omega C}} = \frac{1}{R_1 + j\omega L} + \frac{j\omega C}{j\omega R_2 C + 1}$$

$$Y_{in} = \frac{R_1 - j\omega L}{R_1^2 + (\omega L)^2} + \frac{j\omega C (1 - j\omega R_2 C)}{1 + \omega^2 R_2^2 C^2}$$

For Y_{in} to be real, its imaginary part must be zero

$$\Rightarrow \frac{\omega L}{R_1^2 + (\omega L)^2} = \frac{\omega C}{1 + \omega^2 R_2^2 C^2}$$

$$\Rightarrow \frac{L}{C} = \frac{R_1^2 + (\omega L)^2}{1 + \omega^2 R_2^2 C^2}$$

$$\Rightarrow L + \omega^2 R_2^2 L C^2 = R_1^2 C + C \omega^2 L^2$$

$$\Rightarrow L - R_1^2 C = C\omega^2 L^2 - \omega^2 R_2^2 LC^2$$

$$\Rightarrow \omega^2 = \frac{L - R_1^2 C}{L^2 C - R_2^2 LC^2}$$

$$\Rightarrow \omega^2 = \frac{L - R_1^2 C}{LC(L - R_2^2 C)}$$

$$\Rightarrow \omega^2 = \frac{1}{LC} \quad [\text{Since, } R_1 = R_2]$$


$$\Rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(100\pi)^2 \times 7 \times 10^{-3}} = 1.44 \text{ mF}$$

Hence, the correct answer is 1.44.

Question 47


[Network Theory, Transient]

The RL circuit with $R = 10 \text{ k}\Omega$ and $L = 1 \text{ mH}$ is excited by a step current $I_0 u(t)$. At $t = 0^-$, there is a current $I_L = I_0/5$ flowing through the inductor. The minimum time taken for the current through the inductor to reach 99% of its final value is _____ μs (rounded off to two decimal places).

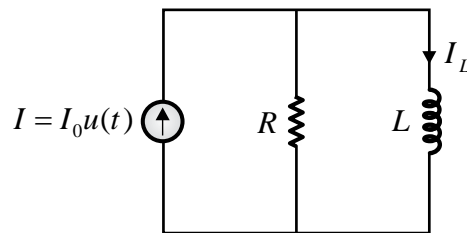


Ans. 0.438 (0.43 to 0.45)

Sol. Given circuit is shown below,

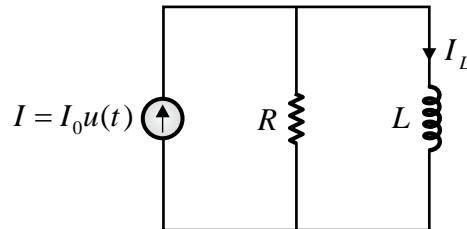

Given : $I_L(0^-) = \frac{I_0}{5}$, $R = 10 \text{ k}\Omega$ and $L = 1 \text{ mH}$

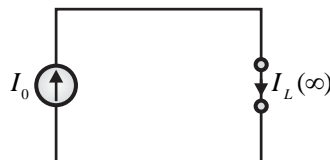At $t \rightarrow \infty$, inductor act as short circuit,



$$I_L(\infty) = I_0$$

$$\text{Time constant } \tau = \frac{L}{R} = \frac{10^{-3}}{10^4} = 10^{-7} \text{ sec}$$

Current in the inductor is given by,

$$\begin{aligned} \therefore I_L(t) &= I_L(\infty) + [I_L(0^-) - I_L(\infty)]e^{-\frac{t}{\tau}} \\ &= I_0 + \left[\frac{I_0}{5} - I_0 \right] e^{-10^7 t} = I_0 - \frac{4I_0}{5} e^{-10^7 t} \end{aligned}$$

For minimum time taken by current to reach 99% of its final value,

$$I_L(t) = 0.99I_0 \text{ then } 0.99I_0 = I_0 - \frac{4I_0}{5} e^{-10^7 t}$$

$$\Rightarrow \frac{4}{5} e^{-10^7 t} = 0.01$$

$$\Rightarrow e^{-10^7 t} = 0.0125$$

$$\Rightarrow t = \frac{\ln(0.0125)}{-10^7} = 0.438 \mu\text{sec}$$

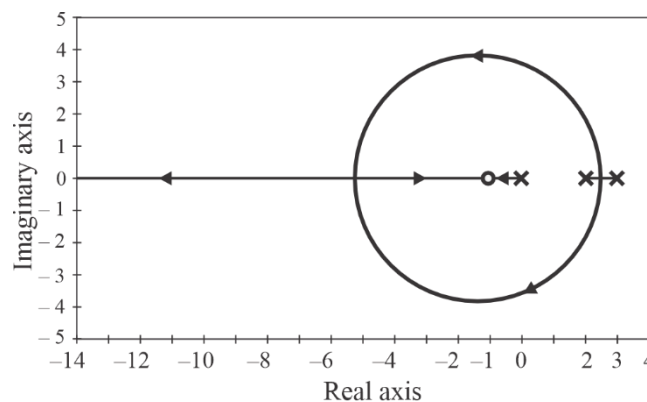
Hence, the correct answer 0.438.

Question 48
[Control System]

Consider a standard negative feedback configuration with $G(s) = \frac{1}{(s-2)(s-3)}$ and the controller

$C(s) = K_p + \frac{K_I}{s} + K_D s$. The root locus of $G(s)C(s)$ is presented in the figure below. The gain

$C(j\omega) = 2$ at $\omega = 1 \text{ rad/s}$. The value of K_D is _____ (rounded off to one decimal place).


Ans. 1 (0.9 to 1.1)

Sol. Given : $G(s) = \frac{1}{(s-2)(s-3)}$ and $C(s) = K_p + \frac{K_I}{s} + K_D s$

$$G(s)C(s) = \frac{k_p + \frac{k_I}{s} + k_D s}{(s-2)(s-3)}$$

$$G(s)C(s) = \frac{s^2 k_D + s k_p + k_I}{s(s-2)(s-3)}$$

From the root locus plot, there will be 2 zero's at $s = -1$.

$$\therefore s^2 k_D + s k_P + k_I = (s+1)^2$$

$$\Rightarrow s^2 k_D + s k_P + k_I = s^2 + 2s + 1$$

$$\therefore \text{On comparison we get } k_D = 1$$

Hence, the correct answer is 1.

Question 49**[Engineering Mathematics, Probability & Statics]**

How many five digit numbers can be formed using the integers 3, 4, 5 and 6 with exactly one digit appearing twice?

Ans. 240 (240 to 240)**Sol. Given :** Integers are 3, 4, 5 and 6, we have to form a five digit number using the given digits.

Let digit 3 is repeated twice.

3 3 4 5 6

$$\therefore \text{Number of five digit number that will be formed when digit 3 is repeated} = \frac{5!}{2!} = 60$$

Let digit 4 is repeated twice.

3 4 4 5 6

$$\therefore \text{Number of five digit number that will be formed when digit 4 is repeated} = \frac{5!}{2!} = 60$$

Let digit 5 is repeated twice.

3 4 5 5 6

$$\therefore \text{Number of five digit number that will be formed when digit 5 is repeated} = \frac{5!}{2!} = 60$$

Let digit 6 is repeated twice.

$$\therefore \text{Number of 5 digit number that will be formed when digit 6 is repeated} = \frac{5!}{2!} = 60$$

Total number of 5 digit number that will be formed when a digit is repeated twice will be $60 \times 4 = 240$.

Hence, the correct answer is 240.

Question 50**[Control System, Frequency Response]**

The phase margin of the transfer function $G(s) = \frac{2(1-s)}{(1+s)^2}$ is _____ degrees (rounded off to the nearest integer).

Ans. 0**Sol. Given :** $G(s) = \frac{2(1-s)}{(1+s)^2}$

$$G(j\omega) = \frac{2(1-j\omega)}{(1+j\omega)^2}$$

Phase Margin is given by,

$$PM = 180^\circ + \angle G(j\omega)_{\omega=\omega_{gc}}$$

Gain cross over frequency is given by,

$$|G(j\omega)|_{\omega=\omega_{gc}} = 1$$

$$|G(j\omega)| = \frac{2\sqrt{1+\omega^2}}{(1+\omega^2)}$$

$$\text{At } \omega = \omega_{gc},$$

$$\frac{2\sqrt{1+\omega_{gc}^2}}{(1+\omega_{gc}^2)} = 1$$

$$2\sqrt{1+\omega_{gc}^2} = (1+\omega_{gc}^2)$$

$$2 = \sqrt{1+\omega_{gc}^2}$$

$$4 = 1 + \omega_{gc}^2$$

$$\omega_{gc}^2 = 3$$

$$\omega_{gc} = \sqrt{3} \text{ rad/sec}$$

$$\angle G(j\omega) = -\tan^{-1} \omega - 2 \tan^{-1} \omega = -3 \tan^{-1} \omega$$

$$\text{At } \omega = \omega_{gc},$$

$$\angle G(j\omega_{gc}) = -3 \tan^{-1} \sqrt{3} = -180^\circ$$

$$\text{Phase Margin} = 180^\circ + \angle G(j\omega_{gc}) = 180^\circ - 180^\circ = 0^\circ$$

Hence, the correct answer is 0.

Question 51

A wire-wound 'resistive potentiometer type' angle sensor with 72 turns is used in an application. The first turn of the potentiometer is connected to ground while its last turn is connected to 3.6 V. The width of the wiper covers two turns ensuring make-before-break. The output (wiper) voltage when the wiper is on top of both the turns 35 and 36 is _____ V (rounded off to two decimal places).

Ans. 1.77 (1.77 to 1.78)

Question 52

[Measurement]

The two secondaries of a linear variable differential transformer (LVDT) showed a magnitude of 2 V (RMS) for zero displacement position of the core. It is noted that the phase of one of the secondaries has a deviation of one degree from the expected phase. Other than this deviation, the LVDT is ideal.

If the differential output sensitivity of the LVDT is 1 mV (RMS)/1 μm , the output for zero displacement is _____ μm (rounded off to one decimal place).

Ans. 34.9 (34.5 to 35.5)

Sol. Zero disp

$$V_1 = 2\angle 0$$

$$V_2 = 2\angle 1^\circ$$

$$V_0 = V_1 - V_2$$

$$V_0 = [2^2 + 2^2 - 2 \times 2 \times 2 \cos 1^\circ]^{1/2} = 2\sqrt{2}(1 - \cos 1^\circ)^{1/2}$$

$$V_0 = 2\sqrt{2} \times \sqrt{2} \sin 0.5 = 34.9 \text{ mV}$$

$$S = 1 \text{ mV}/\mu\text{V}$$

$$\text{disp} = 34.9 \mu\text{m}$$

Hence, the correct answer is 34.9.

Question 53

[Measurement, Error]

Five measurements are made using a weighing machine, and the readings are 80 kg, 79 kg, 81 kg, 79 kg and 81 kg. The sample standard deviation of the measurement is _____ kg (rounded off to two decimal places).

Ans. 1 (0.98 to 1.02)

Sol. Given : Measurements are 80 kg, 79 kg, 81 kg, 79 kg and 81 kg.
The sample standard deviation is given as,

$$\sigma = \sqrt{\frac{1}{N-1} \sum_{i=1}^N [x_i - \bar{x}]^2} \quad \text{where, } N = 5$$

$$\bar{x} = \frac{80 + 79 + 81 + 79 + 81}{5} = 80$$


$$\begin{aligned} \sigma &= \sqrt{\frac{1}{4} [(80-80)^2 + (79-80)^2 + (81-80)^2 + (79-80)^2 + (81-80)^2]} \\ &= \sqrt{\frac{1}{4} [0 + 1 + 1 + 1 + 1]} = 1 \end{aligned}$$

Hence, the correct answer is 1.

Question 54

[Measurement, Bridge]



Four strain gauges R_A , R_B , R_C and R_D , each with nominal resistance R , are connected in a bridge configuration. When a force is applied, R_A and R_D increase by ΔR and R_B and R_C decrease by ΔR as shown. A potentiometer with total resistance R_V is connected as shown. If $R = 100 \Omega$ and $\Delta R = 1 \Omega$, the minimum value of resistance R_V required to balance the bridge is _____ Ω . (rounded off to two decimal places)

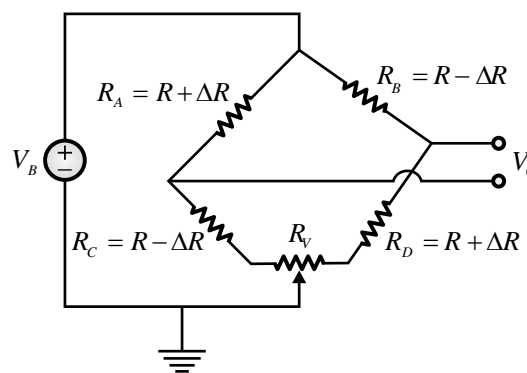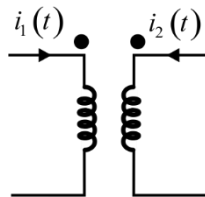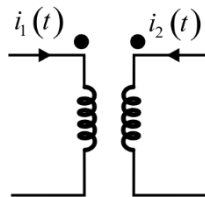

Ans. 4.04 (4.00 to 4.10)

Question 55**[Network Theory, Magnetic Coupled Circuit]**

A sinusoidal current of $i_1(t) = 1\sin(200\pi t)$ mA is flowing through a 4 H inductor which is mutually coupled to another 5 H inductor carrying $i_2(t) = 2\sin(200\pi t)$ mA as shown in figure. The coupling coefficient between the inductors is 0.6. The peak energy stored in the circuit is _____ μJ (rounded off to two decimal places).

**Ans. 17.37 (17.00 to 18.00)****Sol.** Given : Coupled circuit is shown below,

$$i_1(t) = \sin(200\pi t) \text{ mA}$$

$$i_2(t) = 2\sin(200\pi t) \text{ mA}$$

$$L_1 = 4 \text{ H}$$

$$L_2 = 5 \text{ H}$$

Coupling coefficient $K = 0.6$.

$$\text{Mutual inductance } M = K\sqrt{L_1L_2}$$

$$\Rightarrow M = 0.6 \times \sqrt{5 \times 4}$$

$$\Rightarrow M = 0.6 \times \sqrt{20} = 2.683$$

 \therefore Peak value of energy will be,


$$E_p = \frac{1}{2} \times 4 \times 1^2 + \frac{1}{2} \times 5 \times 2^2 + 2.683 \times 1 \times 2$$

$$E_p = 2 + 10 + 5.366 = 17.366 \mu\text{J}$$

Hence, the correct answer is 17.366


Question 56

The figure below shows a feedback amplifier constructed using an nMOS transistor. Assume that $\mu_n C_{ox} = 1 \text{ mA/V}^2$, threshold voltage $V_T = 1 \text{ V}$ and $W/L = 2$. The bias voltage at the drain terminal is 4 V. The capacitors C_∞ offer zero impedance at the signal frequency. The ratio V_{out}/V_{in} is _____. (rounded off to two decimal places)

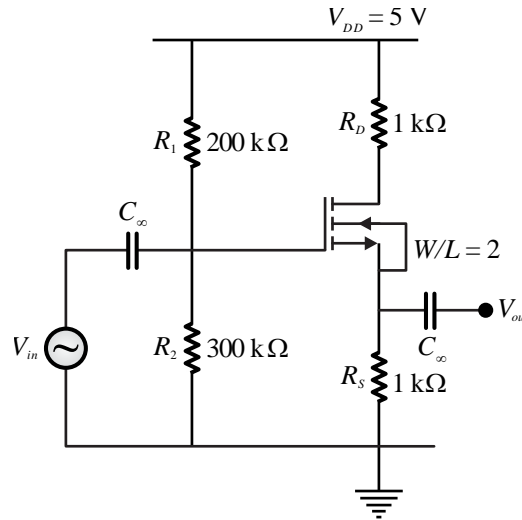


Ans. 0.666 (0.64 to 0.70)

Sol. Given circuit is as shown below,

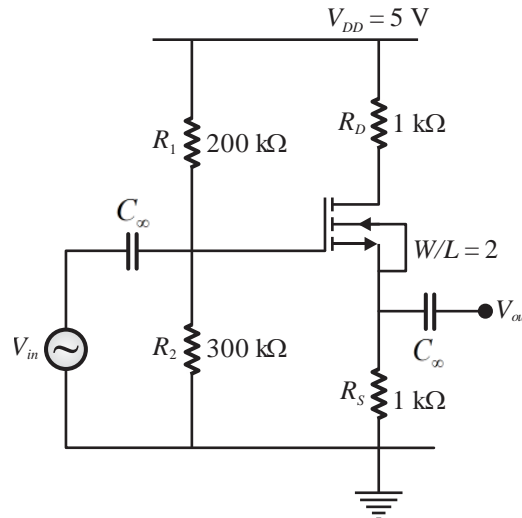

Also given that the bias voltage at the drain terminal is 4 V.

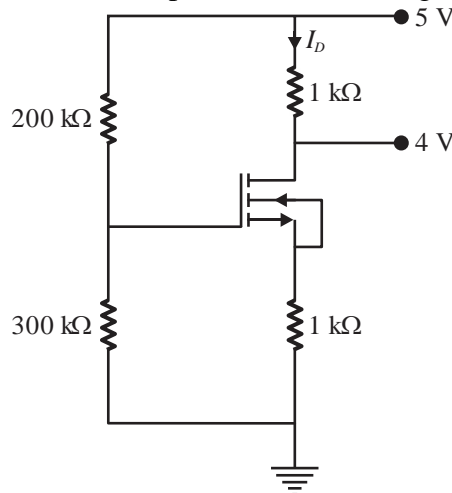For DC analysis, all the capacitors will be open circuit. So, the given circuit becomes as shown below,




$$\text{Drain current, } I_D = \frac{5-4}{1} = 1 \text{ mA}$$

$$\text{Given, } \mu_n C_{ox} = 1 \text{ mA/V}^2, \frac{W}{L} = 2 \text{ and threshold voltage } V_T = 1 \text{ V.}$$

$$\therefore \text{ Transconductance, } g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_m = \sqrt{2 \times 1 \times 10^{-3} \times 2 \times 10^{-3}} = 2 \text{ m}\Omega$$

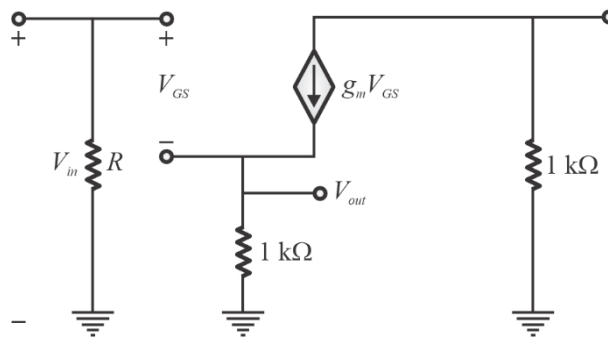For AC analysis, all the capacitors become short circuit and the small signal equivalent model can be drawn as shown below,



$$\text{Here, } R = 200 \text{ k}\Omega \parallel 300 \text{ k}\Omega$$

$$\text{KVL } \Rightarrow V_{in} - V_{GS} - V_{out} = 0$$

$$\text{But } V_{out} = g_m V_{GS} \times 1 \text{ k}\Omega \quad \dots(i)$$

$$V_{in} - V_{GS} - g_m V_{GS} \times 1 \text{ k}\Omega = 0$$

$$V_{in} = V_{GS} [1 + g_m \times 1 \text{ k}\Omega]$$

$$V_{GS} = \frac{V_{in}}{1 + g_m \times 1 \text{ k}\Omega} \quad \dots(ii)$$

Substituting equation (ii) in equation (i), we get

$$V_{out} = \frac{g_m V_{in} \times 1 \text{ k}\Omega}{1 + g_m \times 1 \text{ k}\Omega}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_m \times 1 \text{ k}\Omega}{1 + g_m \times 1 \text{ k}\Omega}$$

$$\text{But } g_m = 2 \text{ m}\Omega,$$

$$\frac{V_{out}}{V_{in}} = \frac{2 \times 10^{-3} \times 10^3}{1 + 2 \times 10^{-3} \times 10^3} = \frac{2}{3} = 0.66$$

Hence, the correct answer is 0.66.

Question 57

[Engineering Mathematics, Maxima & Minima]

Consider the real-valued function $g(x) = \max\{(x-2)^2, -2x+7\}$ where $x \in (-\infty, \infty)$. The minimum value attained by $g(x)$ is _____. (rounded off to one decimal place)

Ans. 1 (0.9 to 1.1)

Sol. Given : $g(x) = \max\{(x-2)^2, -2x+7\}$, where $x \in (-\infty, \infty)$.

The point of intersection of $(x-2)^2$ and $(-2x+7)$ can be obtained as shown below,

$$(x-2)^2 = -2x+7$$

$$x^2 - 4x + 4 = -2x + 7$$

$$x^2 - 2x - 3 = 0$$

$$x^2 - 3x + x - 3 = 0$$

$$x(x-3) + 1(x-3) = 0$$

$$(x-3)(x+1) = 0$$

$$x = 3 \text{ and } x = -1$$

$$\therefore \text{ When } x = 3, g(x) = \max\{1, 1\} = 1$$

$$\text{When } x = -1, g(x) = \max\{9, 9\} = 9$$

Co-ordinates of points of intersection are (3, 1) and (-1, 9).

\therefore Minimum value of $g(x)$ is 1.


Hence, the correct answer is 1.

Question 58**[Machine, Transforms]**

A short-circuit test is conducted on a single-phase transformer by shorting its secondary. The frequency of input voltage is 1 kHz. The corresponding wattmeter reading, primary current and primary voltage are 8 W, 2 A & 6 V respectively. Assume that the no-load losses & the no-load currents are negligible, and the core has linear magnetic characteristics. Keeping the secondary shorted, the primary is connected to a 2 V (rms), 1 kHz sinusoidal source in series with $\frac{1}{2\pi\sqrt{5}}$ mF capacitor. The primary current (rms) will be _____ A. (rounded off to two decimal places)


Ans. 1 (0.95 to 1.05)**Question 59**

The Op-Amps in the circuit are ideal. The input signals are $V_{s1} = 3 + 0.1\sin(300t)$ V and $V_{s2} = -2 + 0.11\sin(300t)$ V. The average value of voltage V_0 is _____ V. (rounded off to two decimal places).

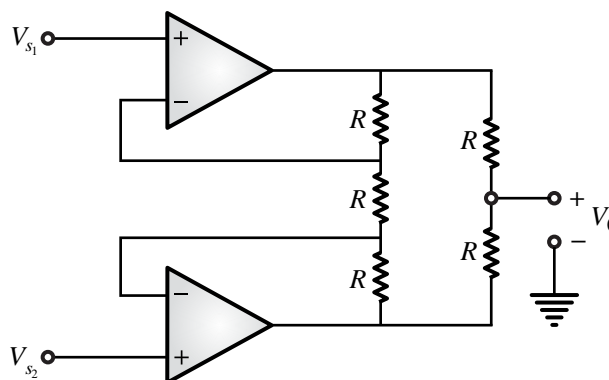

Ans. 0.5 (0.49 to 0.51)

Sol. Given circuit is as shown below,

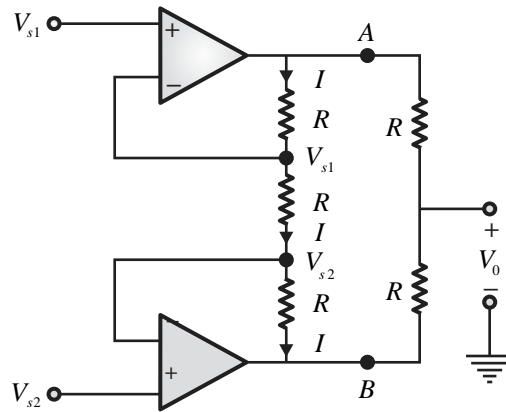

Using voltage division rule and superposition theorem, we get

$$\Rightarrow V_0 = \frac{V_A \times R}{2R} + \frac{V_B \times R}{2R}$$

$$\Rightarrow V_0 = \frac{V_A}{2} + \frac{V_B}{2} = \frac{V_A + V_B}{2}$$

$$\Rightarrow V_0 = \frac{IR + V_{s1} + V_{s2} - IR}{2} \quad (\because V_A = IR + V_{s1}, V_B = V_{s2} - IR)$$

$$\Rightarrow V_0 = \frac{V_{s1} + V_{s2}}{2}$$


$$\Rightarrow (V_0)_{avg} = \frac{(V_{s1})_{avg} + (V_{s2})_{avg}}{2} = \frac{3-2}{2} = 0.5 \quad [\because (V_{s1})_{avg} = 3 \text{ and } (V_{s2})_{avg} = -2]$$

Hence, the correct answer is 0.5.

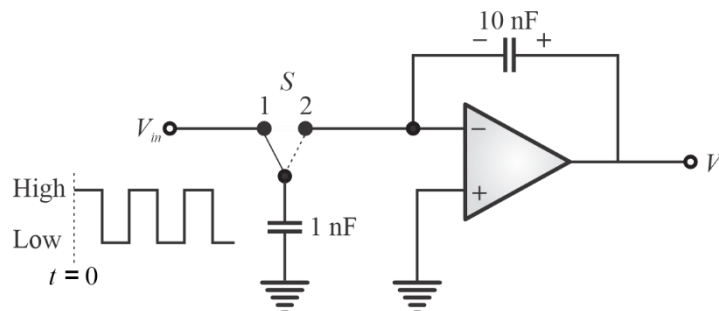Question 60


[Analog Electronics, Op-Amp]

In the circuit shown, the input voltage $V_{in} = 100\text{mV}$. The switch and the op-amp are ideal. At time $t = 0$, the initial charge stored in the 10 nF capacitor is 1 nC , with the polarity as indicated in the figure. The switch S is controlled using a 1 kHz square wave voltage signal V_s as shown. Whenever V_s is 'High', S is in position '1' and when V_s is 'Low', S is in position '2'. At $t = 20\text{ ms}$, the magnitude of the voltage V_0 will be _____ mV (rounded off the nearest integer).



Ans. 100 (99 to 101)

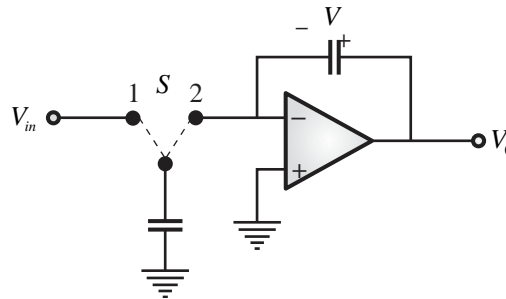Sol. Given circuit can be drawn as shown below,



$$V = \frac{\ln C}{10 \text{ nF}} = 0.1 \text{ V} = 100 \text{ mV}$$

Given frequency of square wave $f = 1 \text{ kHz} \Rightarrow T = 1 \text{ ms}$

At $t = 1 \text{ ms}$, V_{in} will complete 1 cycle and switch will be in position 2.

So, $V_0 = V = 100 \text{ mV}$ at $t = 1 \text{ ms}$


Similarly at $t = 20 \text{ msec}$, $V_0 = V = 100 \text{ mV}$.

Hence, the correct answer is 100.

Question 61

In the diagram shown, the frequency of the sinusoidal source voltage V_s is 50 Hz. The load voltage is 230 V (rms), and the load impedance is $\frac{230}{\sqrt{2}} + j \frac{230}{\sqrt{2}} \Omega$. The value of attenuator $A_1 = \frac{1}{50\sqrt{2}}$. The

multiplier output voltage $V_0 = \frac{V_x V_y}{1V}$, where V_x and V_y are the inputs. The magnitude of the average value of the multiplier output V_0 is _____ V. (round off to one decimal place)

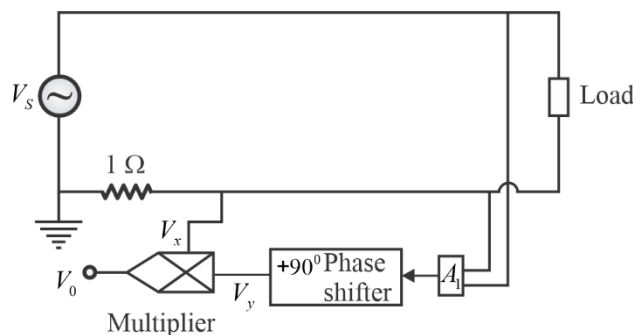


Ans. 2.1 to 2.5

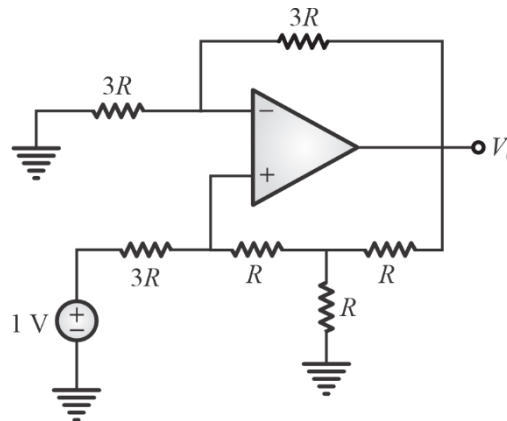Question 62


[Analog Electronics, Op-Amp]

In the circuit shown, assuming an ideal opamp, the value of the output voltage $V_0 = \text{_____ V}$ (rounded off to one decimal place).



Ans. 2 (1.9 to 2.1)

Sol. Circuit is as shown below,

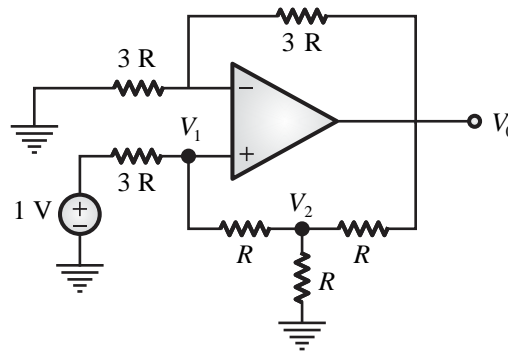

KCL at V_1 ,

$$\frac{V_1 - 1}{3R} + \frac{V_1 - V_2}{R} = 0$$

$$V_1 - 1 + 3V_1 - 3V_2 = 0$$

$$4V_1 - 3V_2 = 1$$

$$V_1 = \frac{1 + 3V_2}{4} \quad \dots(i)$$

KCL at V_2 ,

$$\frac{V_2}{R} + \frac{V_2 - V_0}{R} + \frac{V_2 - V_1}{R} = 0$$

$$3V_2 = V_1 + V_0 \quad \dots(ii)$$

On substituting equation (ii) in equation (i), we get

$$\Rightarrow V_1 = \frac{1}{4} [1 + V_1 + V_0]$$

$$\Rightarrow 3V_1 = V_0 + 1$$

$$\Rightarrow V_1 = \frac{V_0 + 1}{3}$$

$$\therefore V_0 = \left(1 + \frac{3R_1}{3R}\right) V_1$$

$$\therefore V_0 = \left(1 + \frac{3R}{3R}\right) \times \frac{(V_0 + 1)}{3} = \frac{2}{3} V_0 + \frac{2}{3}$$

$$\Rightarrow \frac{V_0}{3} = \frac{2}{3}$$

$$\Rightarrow V_0 = 2 \text{ V}$$

Hence, the correct option is 2.

Question 63

[Engineering Mathematics, Linear Algebra]

The rank of the matrix A given below is one. The ratio $\frac{\alpha}{\beta}$ is _____. (rounded off to the nearest integer)

$$A = \begin{bmatrix} 1 & 4 \\ -3 & \alpha \\ \beta & 6 \end{bmatrix}$$

Ans. - 8 (- 8 to - 8)

Sol. Given : Rank of A , $\rho(A) = 1$

So, all 2×2 minors are zero,

$$\begin{vmatrix} 1 & 4 \\ -3 & \alpha \end{vmatrix} = 0$$

$$\alpha + 12 = 0$$

$$\alpha = -12$$

$$\begin{vmatrix} 1 & 4 \\ \beta & 6 \end{vmatrix} = 0$$

$$6 - 4\beta = 0$$

$$4\beta = 6$$

$$\beta = \frac{3}{2}$$

$$\frac{\alpha}{\beta} = \frac{-12}{\frac{3}{2}} = -\frac{24}{3} = -8$$

Hence, the correct answer is - 8.

Question 64


A 1.999 V true RMS 3-1/2 digit multi-meter has an accuracy of $\pm 0.1\%$ of reading ± 2 digits. It is used to measure 100 A (RMS) current flowing through a line using a 100:5 ratio, Class-1 current transformer with a burden of $0.1 \Omega \pm 0.5\%$. The worst-case absolute error in the multimeter output is _____ V (rounded off to three decimal places).

Ans. 0.010 (0.009 to 0.011)

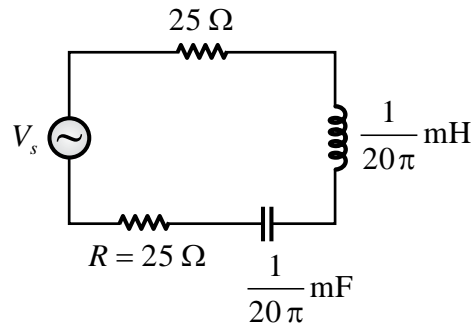Question 65


[Network Theory, AC Analysis]

The voltage source $V_s = 10\sqrt{2} \sin(20000\pi t)$ V has an internal resistance of 50Ω . The RMS value of current through R is _____ mA (rounded off to one decimal places).



Ans. 100 (99.0 to 101.0)

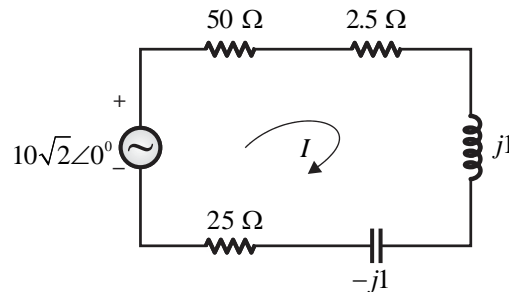Sol. Given circuit can be drawn in phasor form as shown below



$$I = \frac{10\sqrt{2}\angle 0^\circ}{50 + 25 + j1 - j1 + 25}$$

$$I = \frac{10\sqrt{2}}{100} = 100\sqrt{2} \text{ mA}$$

$$\therefore \text{RMS value of current will be, } I_{RMS} = \frac{100\sqrt{2}}{\sqrt{2}} = 100 \text{ mA}$$

Hence, the correct answer is 100.

